
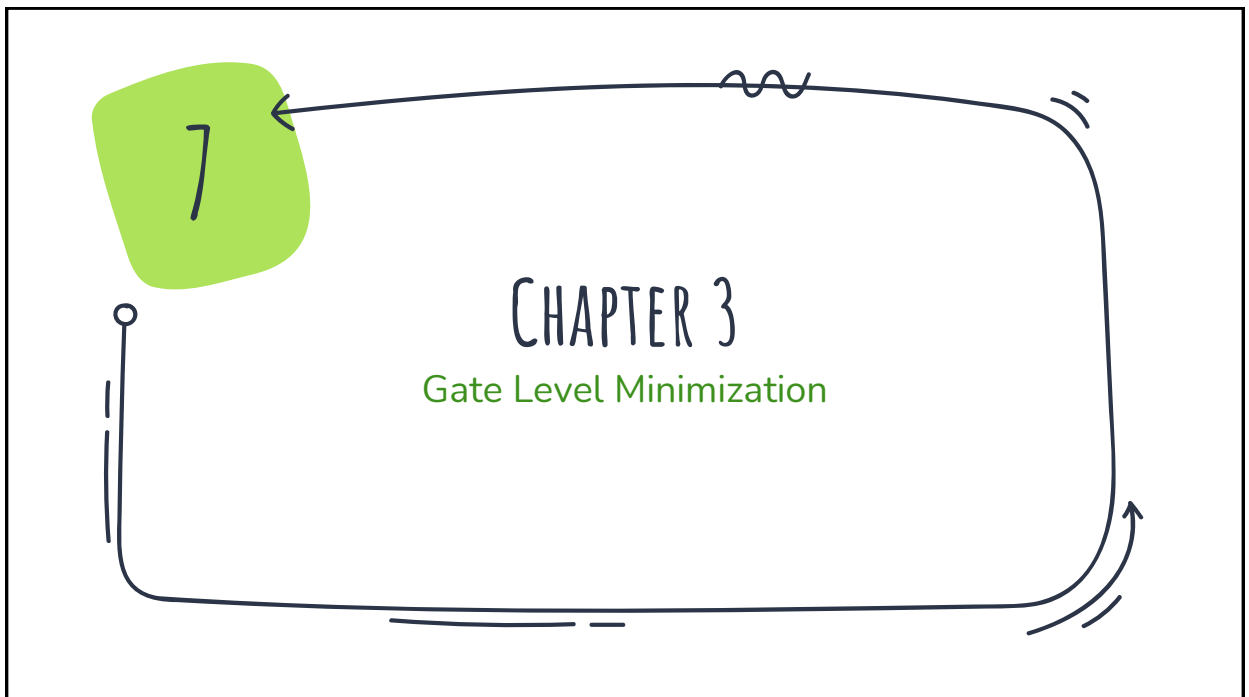


1

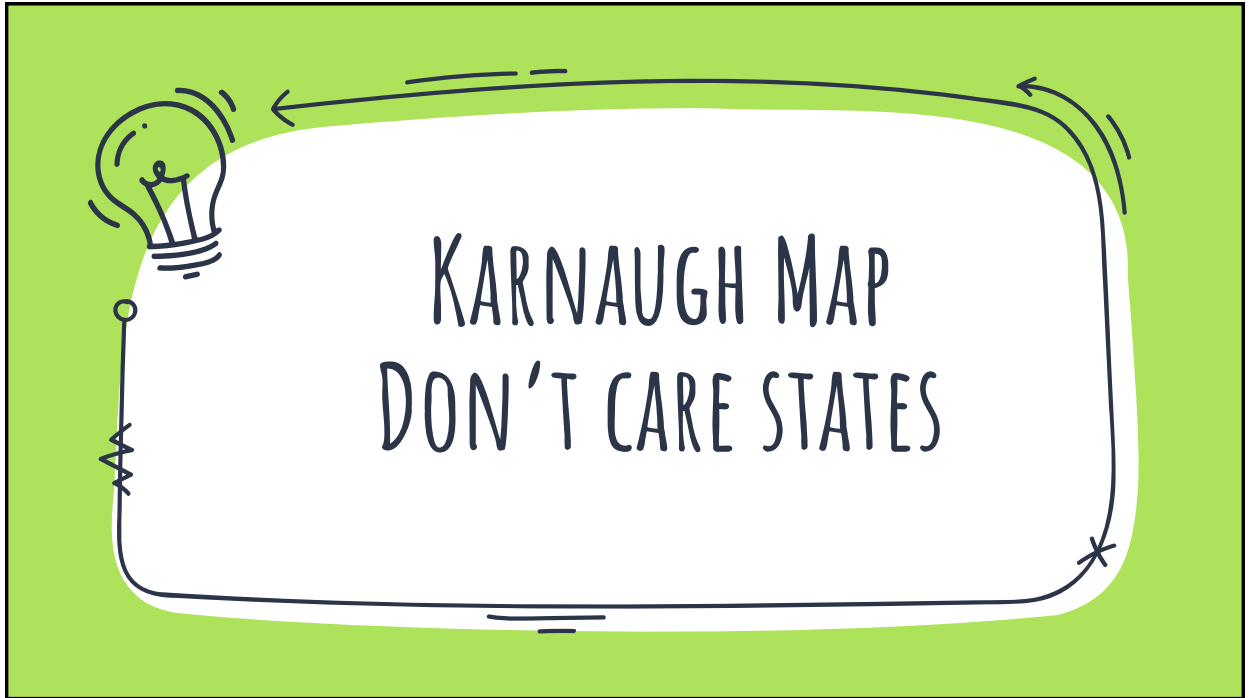

2



4

DON'T CARE STATES

- ✗ You don't always need all 2^n input combinations in an n-variable function;
- ✗ If you can guarantee that certain input combinations never occur
- ✗ If some outputs aren't used in the rest of the circuit

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	1
0	1	0	X
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	X
1	1	1	1

5

DON'T CARE STATES

- X An input-sequence for which the function output does not matter is called don't care.
- X When we do not care either 0 or 1 are used as the sets of inputs. It is such a condition that doesn't make any difference on output.

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	1
0	1	0	X
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	X
1	1	1	1

6

INCOMPLETELY SPECIFIED FUNCTIONS

- X Sometimes a function is not completely specified
 - X For instance, when BCD numbers are handled
- X A BCD number is represented by 4 bits with 6 values undefined
 - X What to do with these unused (undefined) values?
 - X Answer: Use them as **don't care conditions**

Decimal Digit	0	1	2	3	4	5	6	7	8	9
BCD	0000	0001	0010	0011	0100	0101	0110	0111	1000	1001

Note: 1010, 1011, 1100, 1101, 1110, and 1111 are **INVALID CODE!**

7

7

DON'T CARE STATES

- ✕ We mark don't-care outputs in truth tables and K-maps with Xs.
- ✕ Within a K-map, each X can be considered as either 0 or 1. You should pick the interpretation that allows for the most simplification.

x	y	z	f(x,y,z)
0	0	0	0
0	0	1	1
0	1	0	X
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	X
1	1	1	1

8

DON'T CARE STATES

$$f(A,B,C,D) = m(1,3,5,7,9) + d(6,8,9)$$

		C			
		00	01	11	10
A	00	0	1	1	0
	01	0	1	1	X
	11	0	1	0	0
	10	X	X	0	0
		D			
		0	1	0	1

$$f = A'D + BC'D \quad \text{without don't cares}$$

$$f = A'D + C'D \quad \text{with don't cares}$$

9

EXAMPLE

Simplify the Boolean function

$$F(w, x, y, z) = \Sigma(1, 3, 7, 11, 15)$$

that has the don't-care conditions

$$d(w, x, y, z) = \Sigma(0, 2, 5)$$



11

11

		yz			
		00	01	11	10
wx	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		z			

$$(a) F = yz + w'x'$$

		yz			
		00	01	11	10
wx	00	X	1	1	X
	01	0	X	1	0
	11	0	0	1	0
	10	0	0	1	0
		z			

$$(b) F = yz + w'z$$



12

12

X What should be the valid answer:

A \ BC	00	01	11	10
0	0	0	0	0
1	0	1	*	*

$$\text{Out} = \bar{A} \bar{B} C$$

A \ BC	00	01	11	10
0	0	0	0	0
1	0	1	*	*

$$\text{Out} = A C$$

A \ BC	00	01	11	10
0	0	0	0	0
1	0	1	*	*


X Ans:

13


13



14

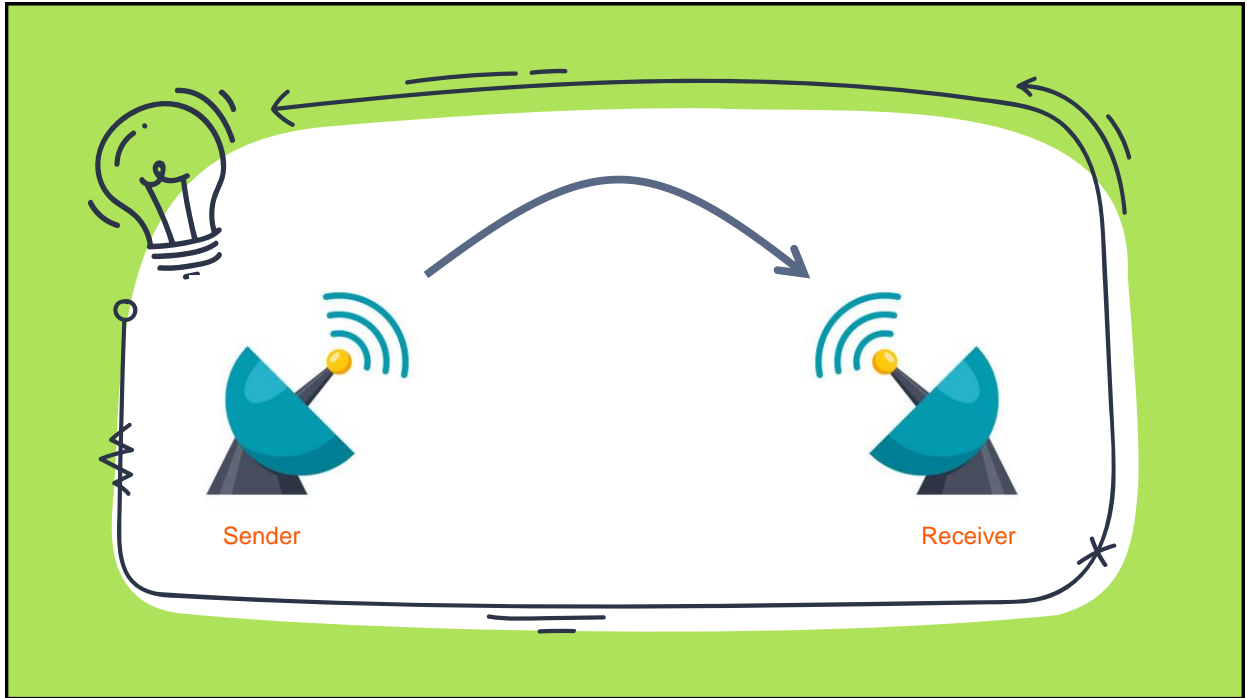


15

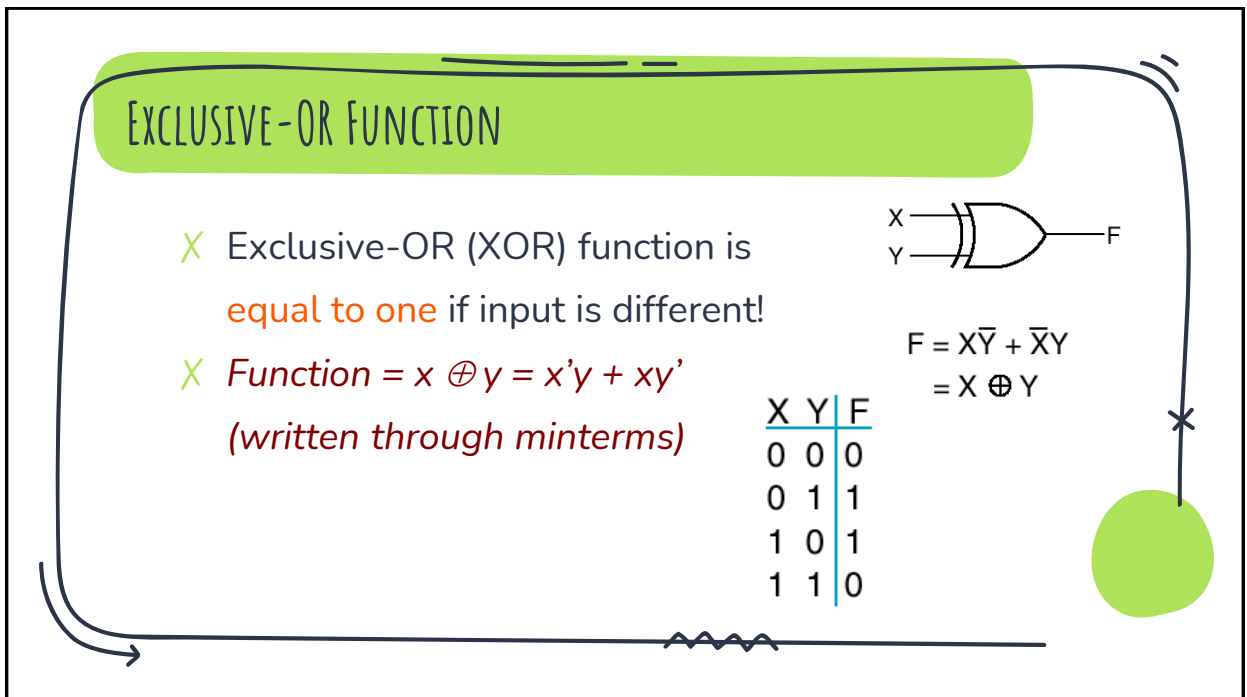

16


REMEMBER 3-INPUT XOR?



$$F = X \oplus Y \oplus Z$$


X Do you see a pattern?

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

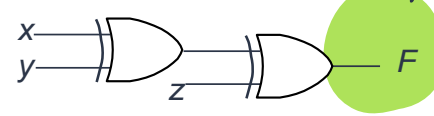

20

REMEMBER 3-INPUT XOR?




$$F = X \oplus Y \oplus Z$$

X Can you get min-terms from this table?

X $A \oplus B \oplus C = A'B'C + A'BC' + AB'C' + ABC$

X $= \Sigma(1, 2, 4, 7)$

X	Y	Z	F
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

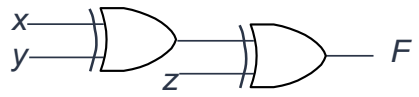

21

IT'S AN ODD FUNCTION!

X $A \oplus B \oplus C = AB'C' + A'BC' + ABC + A'B'C = \Sigma(1, 2, 4, 7)$

X XOR is a odd function \rightarrow an odd number of 1's, then $F = 1$.

X XNOR is a even function \rightarrow an even number of 1's, then $F = 1$.

A \ BC	B			
	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_4	m_5	m_7	m_6
		1		1
	1		1	

(a) Odd function $F = A \oplus B \oplus C$


A \ BC	B			
	00	01	11	10
0	m_0	m_1	m_3	m_2
1	m_4	m_5	m_7	m_6
	1		1	
		1		1

(b) Even function $F = (A \oplus B \oplus C)'$


22

XOR & XNOR

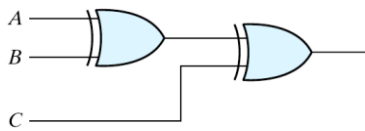X Logic diagrams of odd and even functions



(a) 3-input odd function

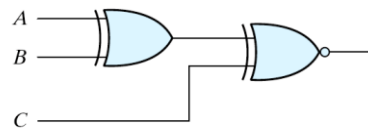

(b) 3-input even function

Logic Diagrams of Odd and Even Functions

23

PARITY - RECALL

X What was parity? (In chapter 1)

Three-Bit Message			Parity Bit
x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Even Parity

24

PARITY GENERATION & CHECKING

X XOR functions are very useful in systems requiring error-detection and correction codes.


X A circuit that generates a parity bit is called a **parity generator**.

X The circuit that checks the parity is called a **parity checker**.


Three-Bit Message			Parity Bit
x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Even Parity

25

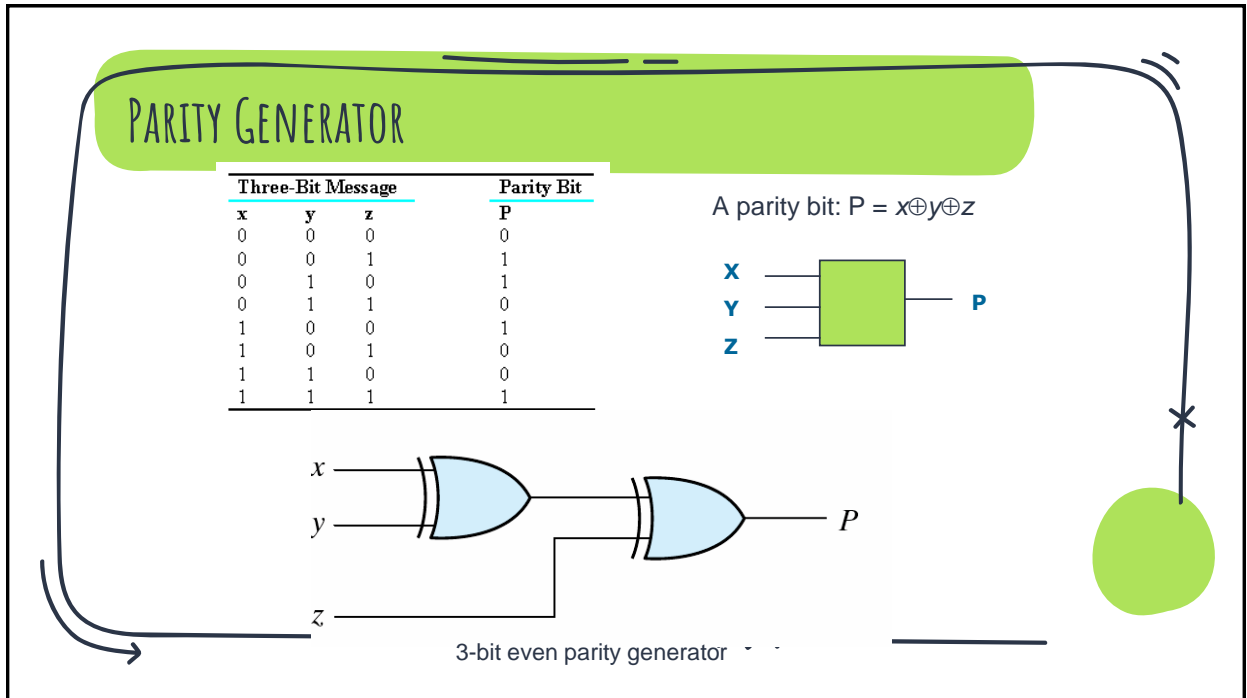


26

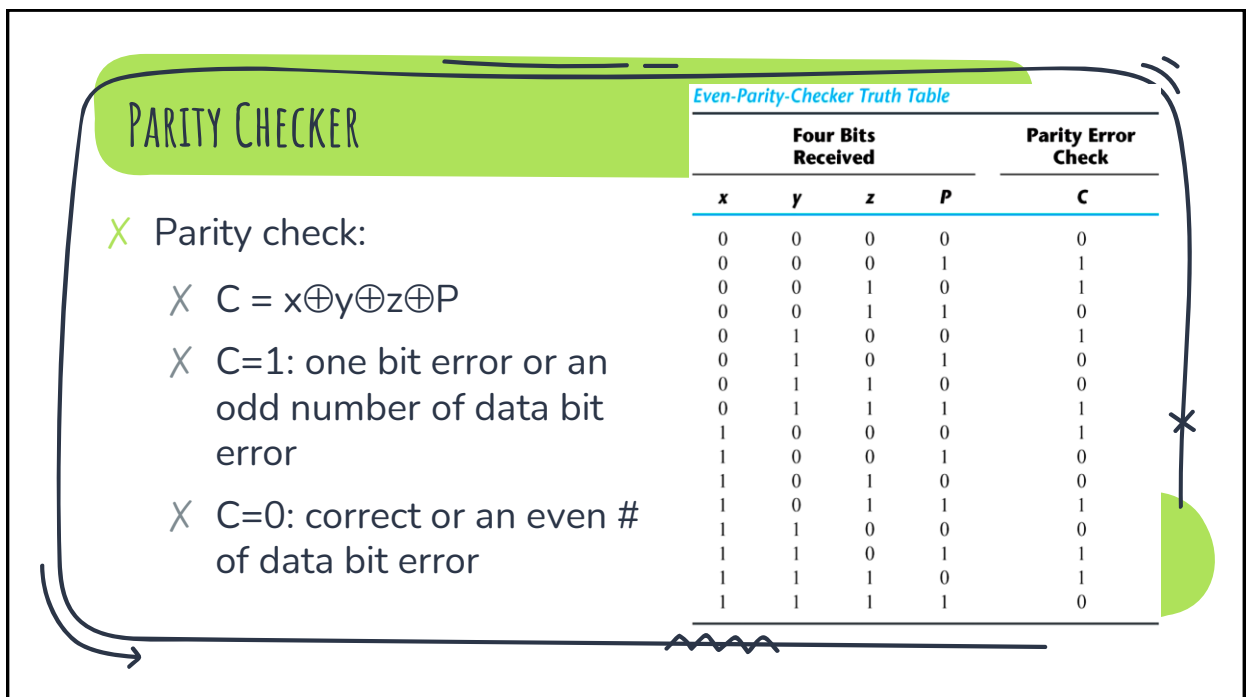

27

PARITY CHECKER

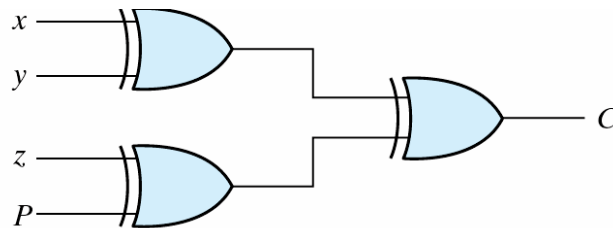- Parity check: $C = x \oplus y \oplus z \oplus P$
 - $C=1$: one bit error or an odd number of data bit error
 - $C=0$: correct or an even # of data bit error



Parity checker

28

REFERENCES

- X Chapter 3 – Digital Design Morris Mano
- X Template is taken from slides carnival.

29