
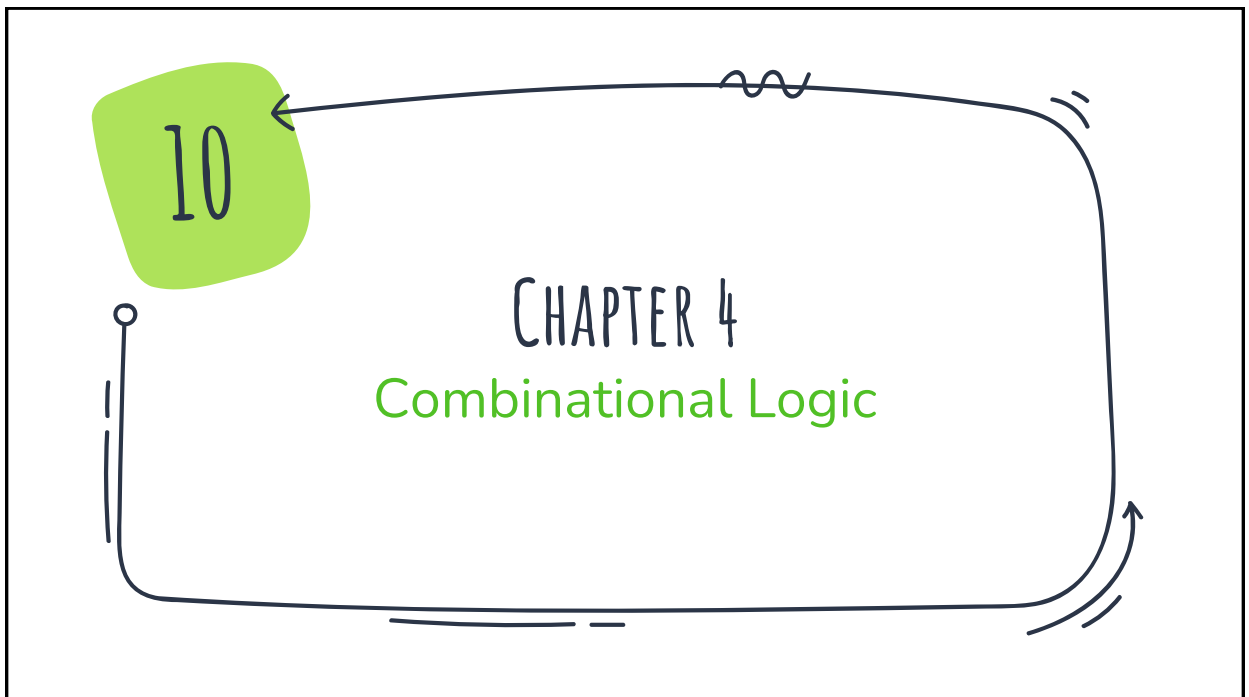


1

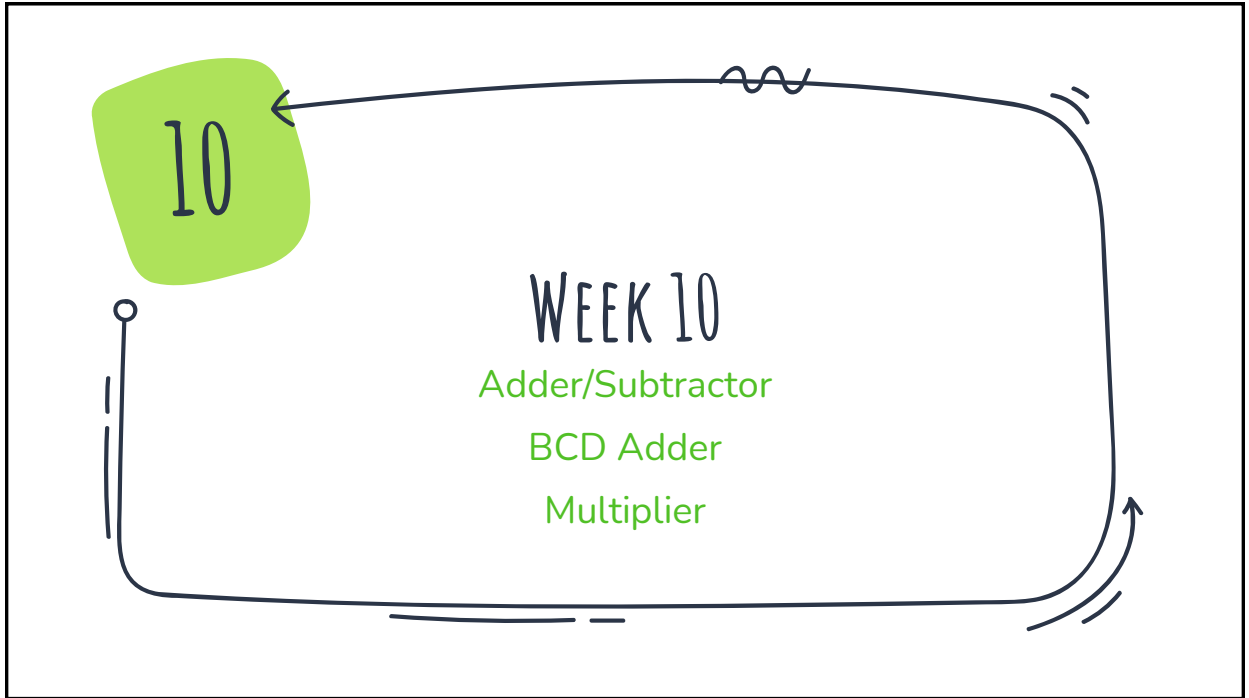


2




3




4

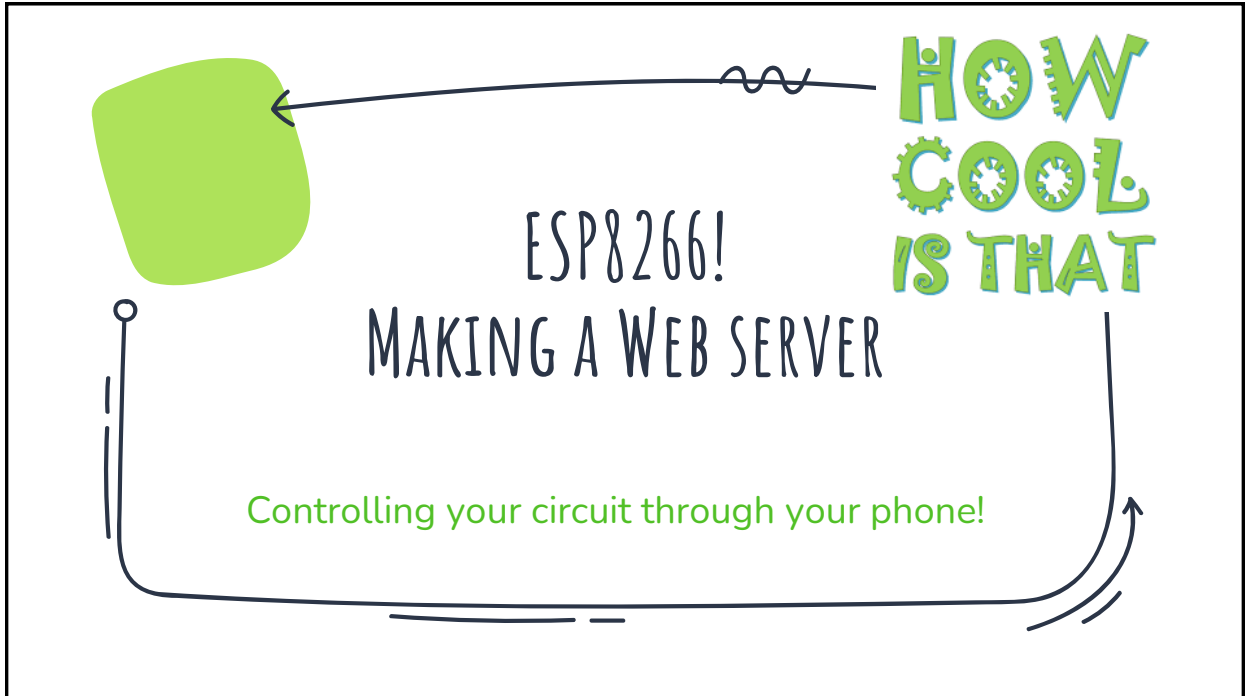


5

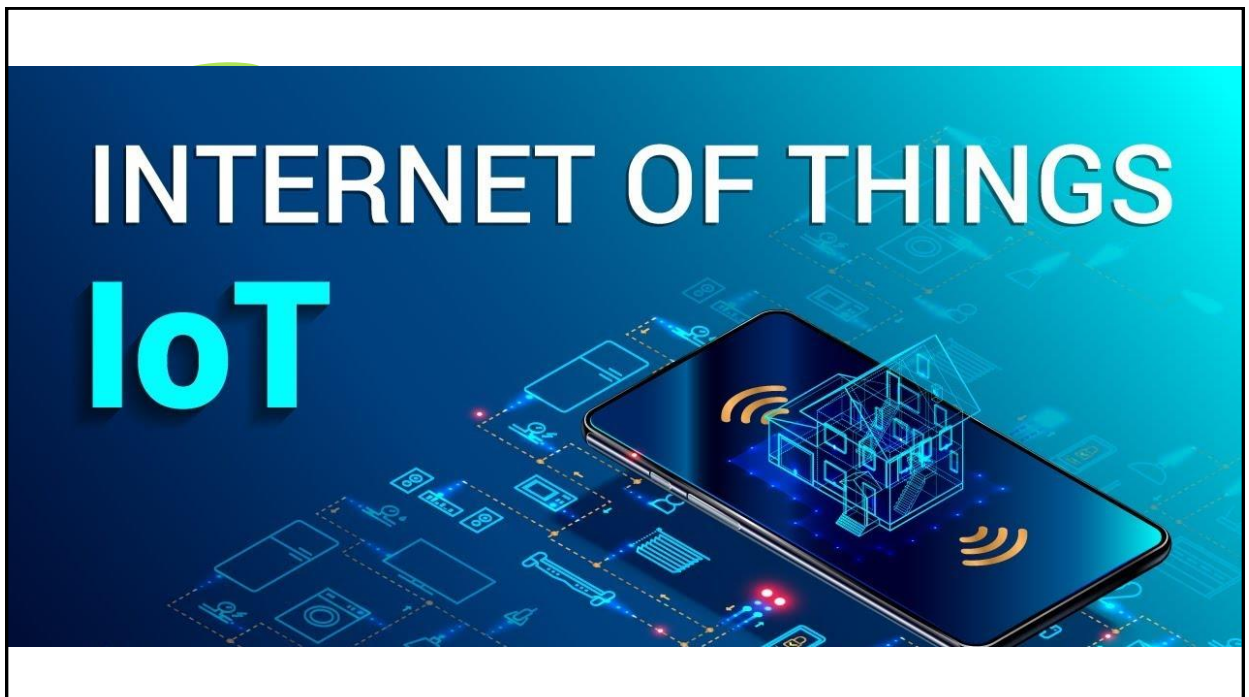

6

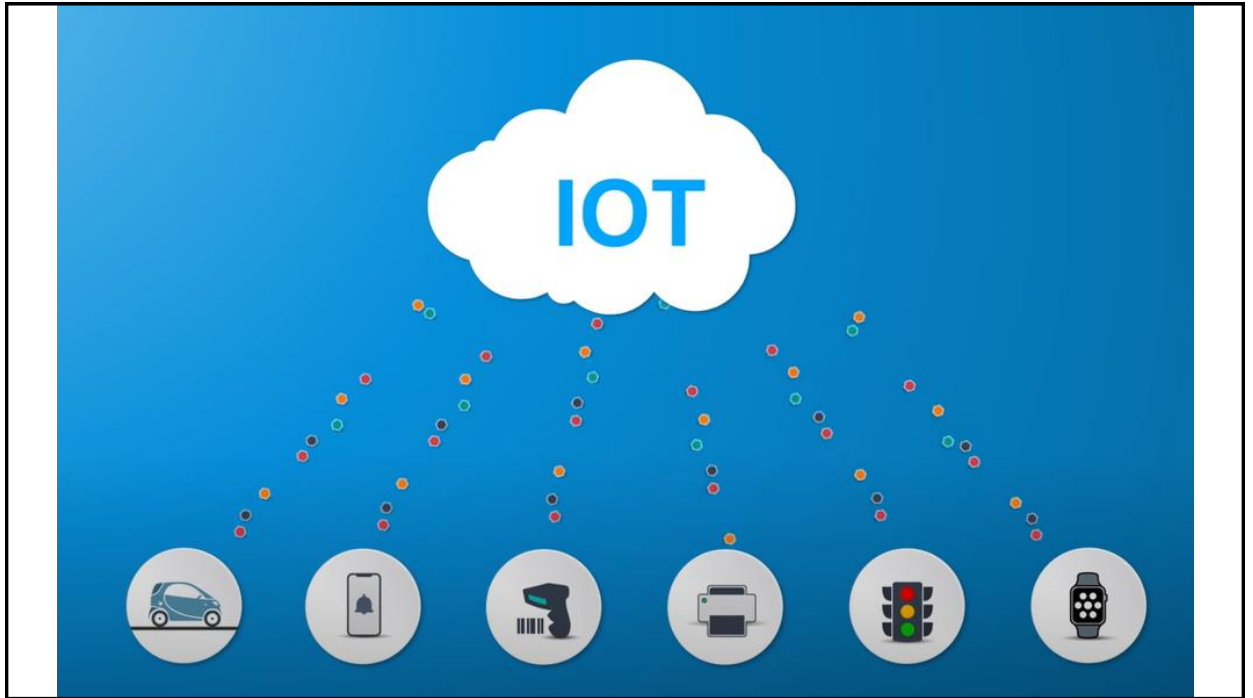


7

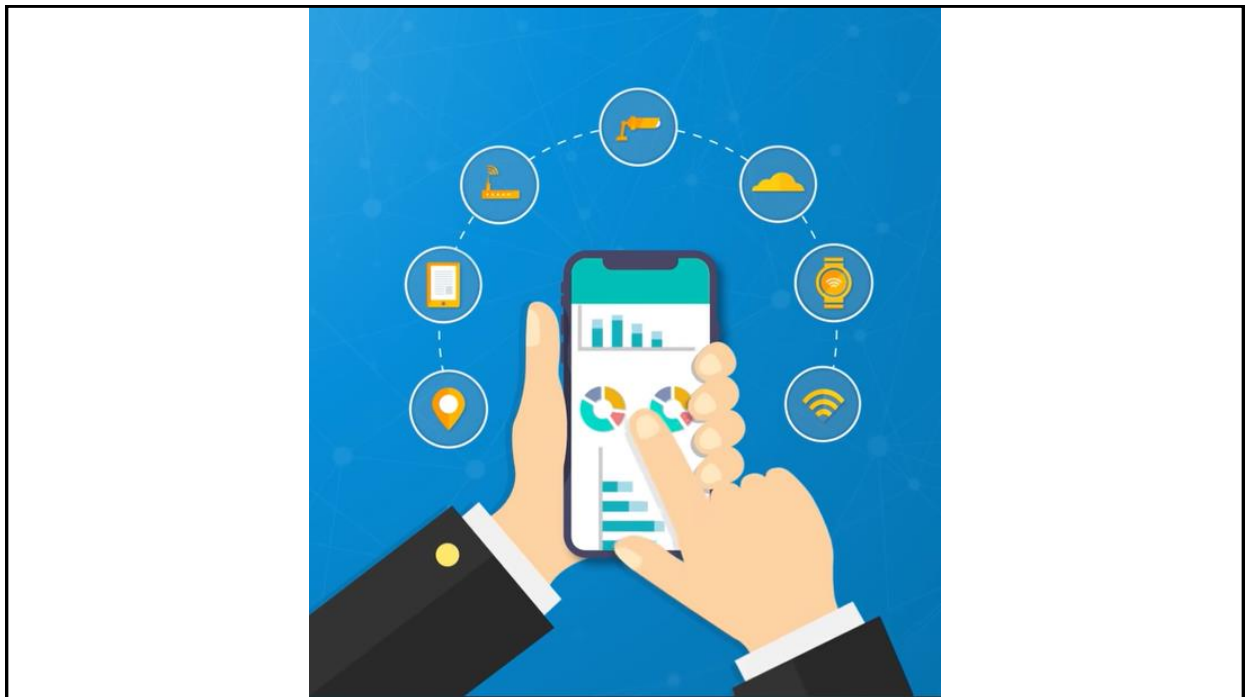

8

MATERIAL TO BE USED IN IOT LAB

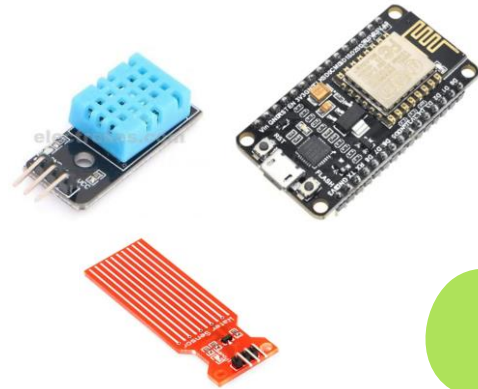- X ESP8266 V3 (550/-)
- X ESP8266 V2 (650/-)
- X DHT11 (240/-)
- X SR04 (170/-)
- X Water Level Sensor (70/-)



9

Binary Adder/ Subtractor

10

Review complements:

- X The subtraction of unsigned binary numbers can be done by complements.
- X 1's complement can be formed by changing 1's to 0's and 0's to 1's
- X 2's complement of a number is done by Taking the 1's complement and adding 1 to the least significant bit in the number.

11

11


BINARY ADDER/SUBTRACTOR

- X How can we implement subtraction?
 - X Subtraction is addition of complement
 - X $N - M = N + (\text{two's complement of } M)$
- X How do we determine 2's complement?
 - X 1's complement (flip bits) and add 1
- X How can we flip bits?
 - X NOT gate (subtraction only)
 - X XOR gate (to provide control: Add/Sub):
 - $x \oplus 0 = x$ (use for Add)
 - $x \oplus 1 = x'$ (use for Sub)
- X How can we add 1?
 - Input carry

12

12

BINARY ADDER/SUBTRACTOR

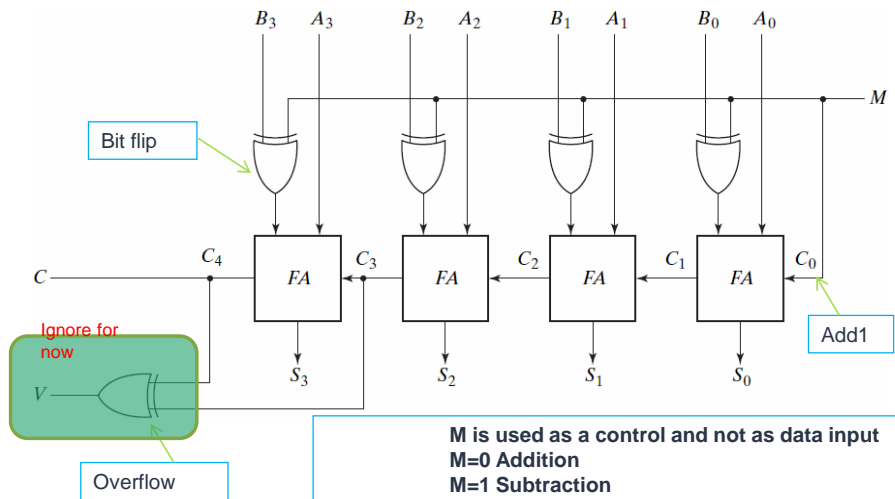

13

13

Binary Adder/Subtractor


M controls the operation (addition or subtraction)

$M = 0 \rightarrow$ Adder: A plus B , $C_0 = 0$

$B \otimes 0 = (B \cdot 1) + (B' \cdot 0) = B$

$M = 1 \rightarrow$ Adder: A plus 2's complement and a $C_0 = 1 \rightarrow A - B$

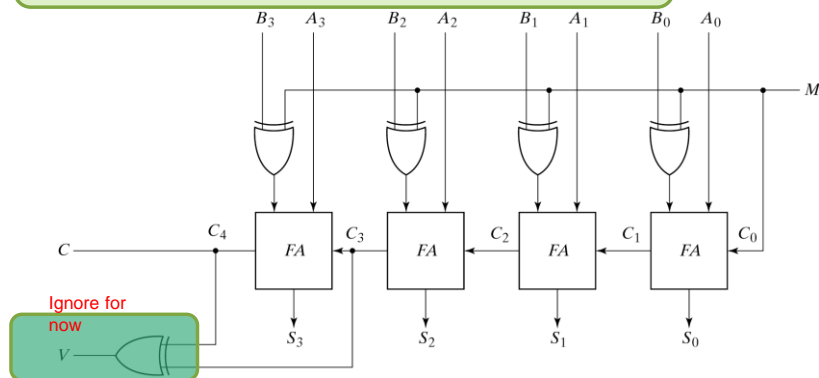$M = 1: B \otimes 1 = (B \cdot 0) + (B' \cdot 1) = B'$



14

14

OVERFLOW

- X n -bit addition can generate $(n+1)$ -bit number
 - X Resulting in “overflow”
 - X Problem: Needs to be detected by computer system
- X How can we detect overflow?
- X For unsigned numbers
 - X End carry out of most significant position
- X For signed numbers
 - X Most significant bit indicates sign
 - X If carry into sign position and out of sign position differ, then overflow
 - X Detected by XOR gate

15

15

OVERFLOW

8 bits can hold signed numbers: -128 to + 127

$$\begin{array}{r}
 80 \\
 -70 \\
 \hline
 +10
 \end{array}
 \quad
 \begin{array}{r}
 1\ 1 \\
 0\ 1\ 0\ 1\ 0\ 0\ 0\ 0 \\
 1\ 0\ 1\ 1\ 1\ 0\ 1\ 0 \\
 \hline
 0\ 0\ 0\ 0\ 1\ 0\ 1\ 0
 \end{array}$$

Overflow cannot occur if one number is positive and other is negative

$$\begin{array}{r}
 70 \\
 -80 \\
 \hline
 -10
 \end{array}
 \quad
 \begin{array}{r}
 0\ 0 \\
 0\ 1\ 0\ 0\ 0\ 1\ 1\ 0 \\
 1\ 0\ 1\ 1\ 0\ 0\ 0\ 0 \\
 \hline
 1\ 1\ 1\ 1\ 0\ 1\ 1\ 0
 \end{array}$$

16

16

OVERFLOW

8 bits can hold signed numbers: -128 to + 127

$$\begin{array}{r}
 +70 \\
 +80 \\
 \hline
 +150
 \end{array}
 \begin{array}{r}
 0 \ 1 \\
 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \\
 0 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \\
 \hline
 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0
 \end{array}$$

×

Overflow may occur when both numbers are positive or both are negative

$$\begin{array}{r}
 -70 \\
 -80 \\
 \hline
 -150
 \end{array}
 \begin{array}{r}
 1 \ 0 \\
 1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 1 \ 0 \\
 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 0 \ 0 \\
 \hline
 0 \ 1 \ 1 \ 0 \ 1 \ 0 \ 1 \ 0
 \end{array}$$

×

17

17

OVERFLOW

$$\begin{array}{r}
 +80 \\
 -70 \\
 \hline
 +10
 \end{array}
 \begin{array}{r}
 1 \ 1 \\
 0 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \\
 1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 1 \ 0 \\
 \hline
 0 \ 0 \ 0 \ 0 \ 1 \ 0 \ 1 \ 0
 \end{array}$$

$$\begin{array}{r}
 +70 \\
 -80 \\
 \hline
 -10
 \end{array}
 \begin{array}{r}
 0 \ 0 \\
 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \\
 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 0 \ 0 \\
 \hline
 1 \ 1 \ 1 \ 1 \ 0 \ 1 \ 1 \ 0
 \end{array}$$


$$\begin{array}{r}
 +70 \\
 +80 \\
 \hline
 +150
 \end{array}
 \begin{array}{r}
 0 \ 1 \\
 0 \ 1 \ 0 \ 0 \ 0 \ 1 \ 1 \ 0 \\
 0 \ 1 \ 0 \ 1 \ 0 \ 0 \ 0 \ 0 \\
 \hline
 1 \ 0 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0
 \end{array}$$

$$\begin{array}{r}
 -70 \\
 -80 \\
 \hline
 -150
 \end{array}
 \begin{array}{r}
 1 \ 0 \\
 1 \ 0 \ 1 \ 1 \ 1 \ 0 \ 1 \ 0 \\
 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 0 \ 0 \\
 \hline
 0 \ 1 \ 1 \ 0 \ 1 \ 0 \ 1 \ 0
 \end{array}$$

18

18

OVERFLOW

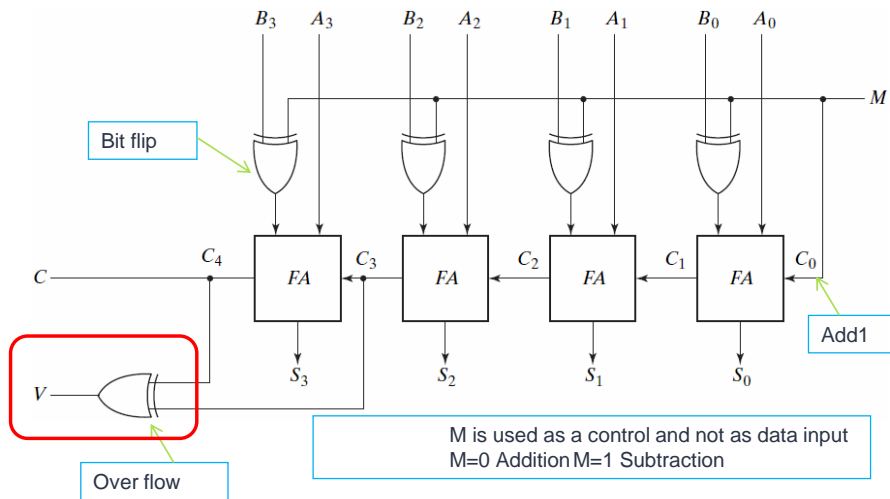

19


19

BCD Adder

20

BCD ADDER

Recal: Conversion & Coding

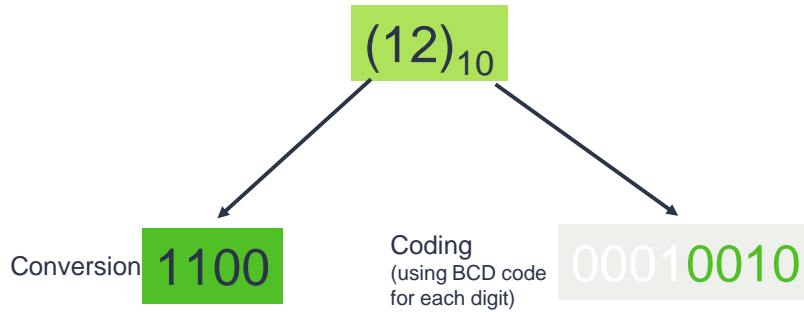

21

21

BCD ADDER

Design a circuit that calculates the Arithmetic addition of two decimal digits.

$$\begin{array}{r}
 9 \\
 + 3 \\
 \hline
 12 \\
 \text{carry}
 \end{array}$$

■ Maximum sum is $9+9 + 1 = 19$

Max digit

Carry from previous digits

22

22

BCD ADDER

- X Full adder \rightarrow (1+1) Bit + 1 Carry= 3 bits
- X BCD \rightarrow (4+4) Bits + 1 Carry= 9 bits input
- X Max output is 9+9+1=19
- X Use 4 bit binary adder
 - X Input 2 BCD numbers
 - X Sum will be in binary form
 - X Output binary number from 0 to 19
 - X AIM: Convert Binary back to BCD

23

23

BCD ADDER

BCD Sum

Number	C	S8	S4	S2	S1
0	0	0	0	0	0
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	0	1	1
4	0	0	1	0	0
5	0	0	1	0	1
6	0	0	1	1	0
7	0	0	1	1	1
8	0	1	0	0	0
9	0	1	0	0	1

Upto 9, the sum of Binary Adder and BCD Adder is same

24

24

BCD ADDER

BCD Sum

Number	C	S8	S4	S2	S1
10	1	0	0	0	0
11	1	0	0	0	1
12	1	0	0	1	0
13	1	0	0	1	1
14	1	0	1	0	0
15	1	0	1	0	1
16	1	0	1	1	0
17	1	0	1	1	1
18	1	1	0	0	0
19	1	1	0	0	1

25

25

BCD ADDER

BCD adder sum

Number	C	S8	S4	S2	S1
10	1	0	0	0	0
11	1	0	0	0	1
12	1	0	0	1	0
13	1	0	0	1	1
14	1	0	1	0	0
15	1	0	1	0	1
16	1	0	1	1	0
17	1	0	1	1	1
18	1	1	0	0	0
19	1	1	0	0	1

Binary sum

K	Z8	Z4	Z2	Z1
0	1	0	1	0
0	1	0	1	1
0	1	1	0	0
0	1	1	0	1
0	1	1	1	0
0	1	1	1	1
1	0	0	0	0
1	0	0	0	1
1	0	0	1	0
1	0	0	1	1

26

26

BCD ADDER

BCD adder sum						Binary sum				
Number	C	S8	S4	S2	S1	K	Z8	Z4	Z2	Z1
10	1	0	0	0	0	0	1	0	1	0
11	1	0	0	0	1	0	1	0	1	1
12	1	0	0	1	0	0	1	1	0	0
13	1	0	0	1	1	0	1	1	0	1
14	1	0	1	0	0	0	1	1	1	0
15	1	0	1	0	1	0	1	1	1	1
16	1	0	1	1	0	1	0	0	0	0
17	1	0	1	1	1	1	0	0	0	1
18	1	1	0	0	0	1	0	0	1	0
19	1	1	0	0	1	1	0	0	1	1

+6

27

27

BCD ADDER

- If sum is up to 9
 - Use the regular Adder.
- If the sum > 9
 - Use the regular adder and add 6 to the result

28

28

BCD Adder

If sum exceeds
binary 9 then
represent it as two
separate binary
numbers

Add binary 6(0110)

Binary Sum					BCD Sum					Dec
K	Z8	Z4	Z2	Z1	C	S8	S4	S2	S1	
0	0	0	0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	2
0	0	0	1	1	0	0	0	1	1	3
0	0	1	0	0	0	0	1	0	0	4
0	0	1	0	1	0	0	1	0	1	5
0	0	1	1	0	0	0	1	1	0	6
0	0	1	1	1	0	0	1	1	1	7
0	1	0	0	0	0	1	0	0	0	8
0	1	0	0	1	0	1	0	0	1	9
0	1	0	1	0	1	0	0	0	0	10
0	1	0	1	1	1	0	0	0	1	11
0	1	1	0	0	1	0	0	1	0	12
0	1	1	0	1	1	0	0	1	1	13
0	1	1	1	0	1	0	1	0	0	14
0	1	1	1	1	1	0	1	0	1	15
1	0	0	0	0	1	0	1	1	0	16
1	0	0	0	1	1	0	1	1	1	17
1	0	0	1	0	1	1	0	0	0	18
1	0	0	1	1	1	1	0	0	1	19

29

29

BCD ADDER – WHEN IS THE SUM > 9

Binary sum

Number	K	Z8	Z4	Z2	Z1
10	0	1	0	1	0
11	0	1	0	1	1
12	0	1	1	0	0
13	0	1	1	0	1
14	0	1	1	1	0
15	0	1	1	1	1
16	1	0	0	0	0
17	1	0	0	0	1
18	1	0	0	1	0
19	1	0	0	1	1

N	K	Z8	Z4	Z2	Z1
0	0	0	0	0	0
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	0	1	1
4	0	0	1	0	0
5	0	0	1	0	1
6	0	0	1	1	0
7	0	0	1	1	1
8	0	1	0	0	0
9	0	1	0	0	1

$$C = K +$$

30

30

BCD ADDER – WHEN IS THE SUM > 9

Binary sum

Number	K	Z8	Z4	Z2	Z1
10	0	1	0	1	0
11	0	1	0	1	1
12	0	1	1	0	0
13	0	1	1	0	1
14	0	1	1	1	0
15	0	1	1	1	1
16	1	0	0	0	0
17	1	0	0	0	1
18	1	0	0	1	0
19	1	0	0	1	1

N	K	Z8	Z4	Z2	Z1
0	0	0	0	0	0
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	0	1	1
4	0	0	1	0	0
5	0	0	1	0	1
6	0	0	1	1	0
7	0	0	1	1	1
8	0	1	0	0	0
9	0	1	0	0	1

$$C = K + Z8*Z4 +$$

31

31

BCD ADDER – WHEN IS THE SUM > 9

Binary sum

Number	K	Z8	Z4	Z2	Z1
10	0	1	0	1	0
11	0	1	0	1	1
12	0	1	1	0	0
13	0	1	1	0	1
14	0	1	1	1	0
15	0	1	1	1	1
16	1	0	0	0	0
17	1	0	0	0	1
18	1	0	0	1	0
19	1	0	0	1	1

N	K	Z8	Z4	Z2	Z1
0	0	0	0	0	0
1	0	0	0	0	1
2	0	0	0	1	0
3	0	0	0	1	1
4	0	0	1	0	0
5	0	0	1	0	1
6	0	0	1	1	0
7	0	0	1	1	1
8	0	1	0	0	0
9	0	1	0	0	1

$$C = K + Z8*Z4 + Z8*Z2$$

32

32

BCD ADDER

Numbers that need correction (add 6) are:

01010 (10)
01011 (11)
01100 (12)
01101 (13)
01110 (14)
01111 (15)
10000 (16)
10001 (17)
10010 (18)
10011 (19)

Decides to add 6?

Adds 6

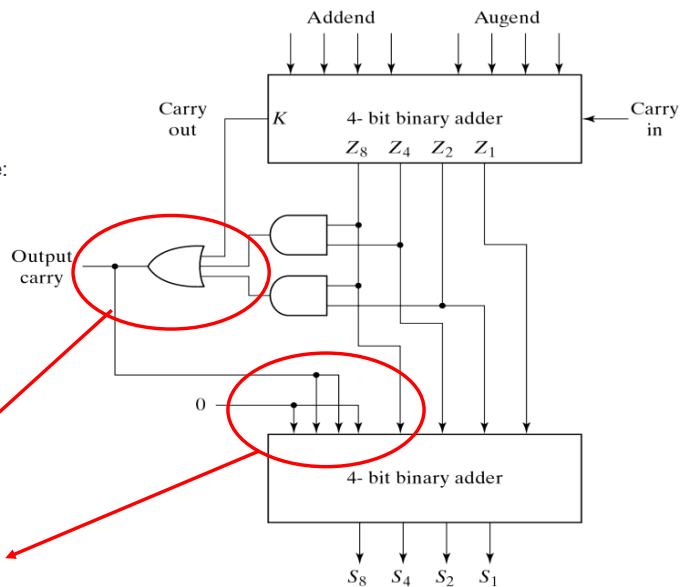


Fig. 4-14 Block Diagram of a BCD Adder

33

33

BCD ADDER

Numbers that need correction (add 6) are:

K Z8 Z4 Z2 Z1

0	1	0	1	0	(10)
0	1	0	1	1	(11)
0	1	1	0	0	(12)
0	1	1	0	1	(13)
0	1	1	1	0	(14)
0	1	1	1	1	(15)
1	0	0	0	0	(16)
1	0	0	0	1	(17)
1	0	0	1	0	(18)
1	0	0	1	1	(19)

$$C = K + Z8Z4 + Z8Z2$$

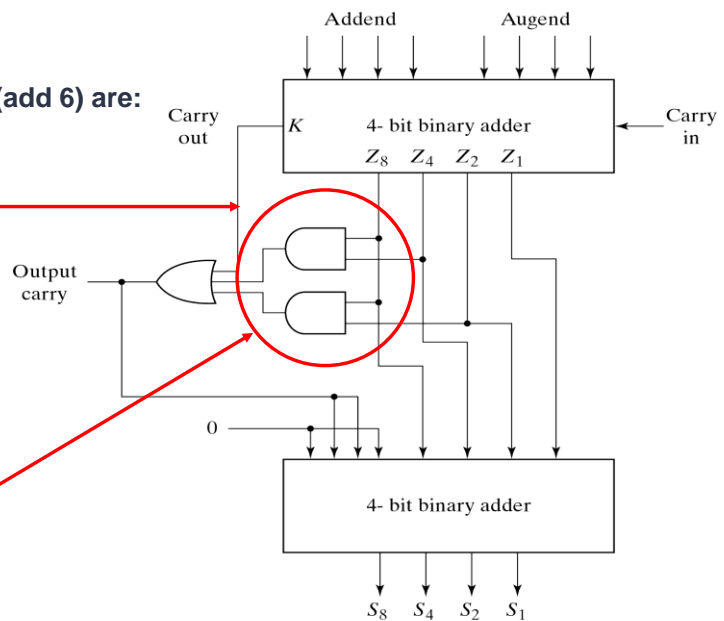


Fig. 4-14 Block Diagram of a BCD Adder

34

34

BINARY MULTIPLIER

- X Multiplication of binary numbers is done in the same way as decimal numbers
- X Multiplicand B is multiplied by the multiplier A starting from the LSB.
- X Successive partial products are shifted one position from the left and the final product is obtained from the sum of partial products.

$$\begin{array}{r}
 \begin{array}{cc} B_1 & B_0 \\ A_1 & A_0 \\ \hline A_0B_1 & A_0B_0 \end{array} \\
 \begin{array}{cc} A_1B_1 & A_1B_0 \\ \hline C_3 & C_2 & C_1 & C_0 \end{array}
 \end{array}$$

35

35

BINARY MULTIPLIER

2-Bit by 2-Bit Binary Multiplier

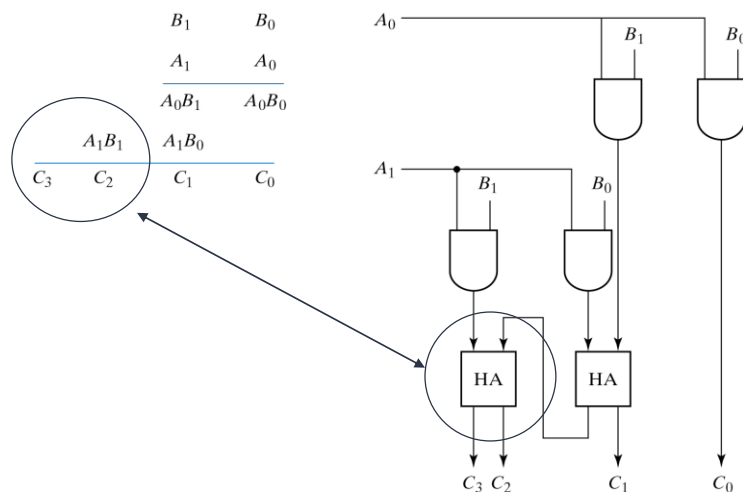


Fig. 4-15 2-Bit by 2-Bit Binary Multiplier

36

36

BINARY MULTIPLIER

B3 B2 B1 B0
A2 A1 A0

A0B3 A0B2 A0B1 A0B0

A1B3 A1B2 A1B1 A1B0

A2B3 A2B2 A2B1 A2B0

$J \times K$

$J \times K$ AND gates
($J-1$) K -bit adders
Result: $J + K$ bits

4-Bit by 3-Bit Binary Multiplier

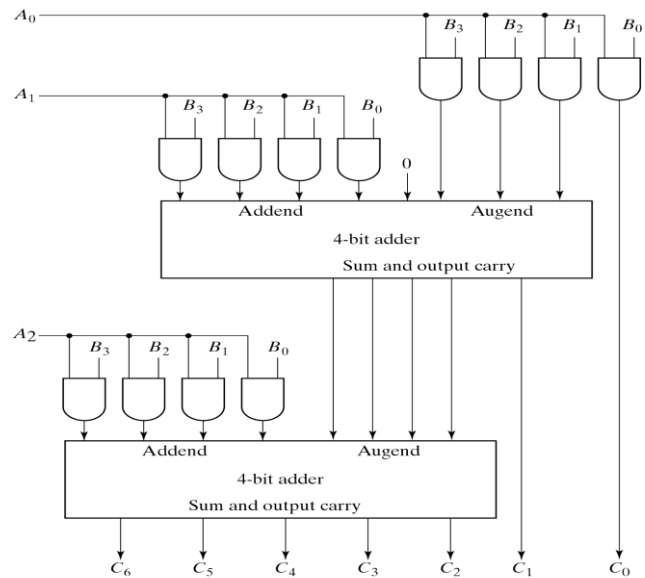


Fig. 4-16 4-Bit by 3-Bit Binary Multiplier

37

37

MULTIPLIER – LAST CLASS QUERIES

✗ 4-bit x 3-bit multiplier

✗ $J=3, K=4$

✗ How many AND gates


✗ $J \times K$ gates

✗ How many adders

✗ ($J-1$) K -bit adders

✗ How many output bits

✗ $J + K$ bits

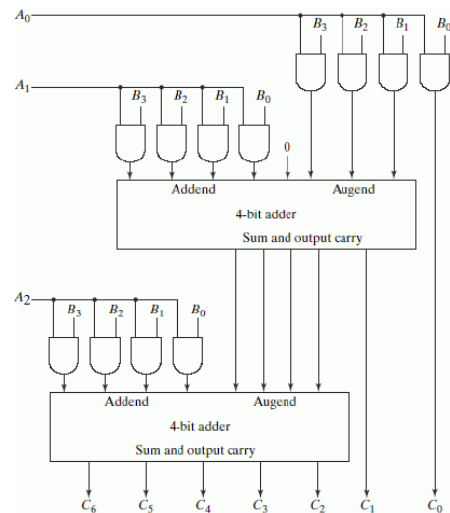

38

PRACTICE EXERCISES


- x Design a 3-bit by 4-bit multiplier
- x Design a 4-bit by 4-bit multiplier

39

39

$K = 4$ $J = 3$ And Gates = $J \times K$ $= 4 \times 3$ $= 12$ Output bits = $J + K$ $= 4 + 3$ $= 7$		<u>MULTIPLIER</u>			
		B_3	B_2	B_1	B_0
			A_2	A_1	A_0
		$A_0 B_3$	$A_0 B_2$	$A_0 B_1$	$A_0 B_0$
	$A_1 B_3$	$A_1 B_2$	$A_1 B_1$	$A_1 B_0$	
	$A_2 B_3$	$A_2 B_2$	$A_2 B_1$	$A_2 B_0$	
C_6	C_5	C_4	C_3	C_2	C_1
					C_0


40

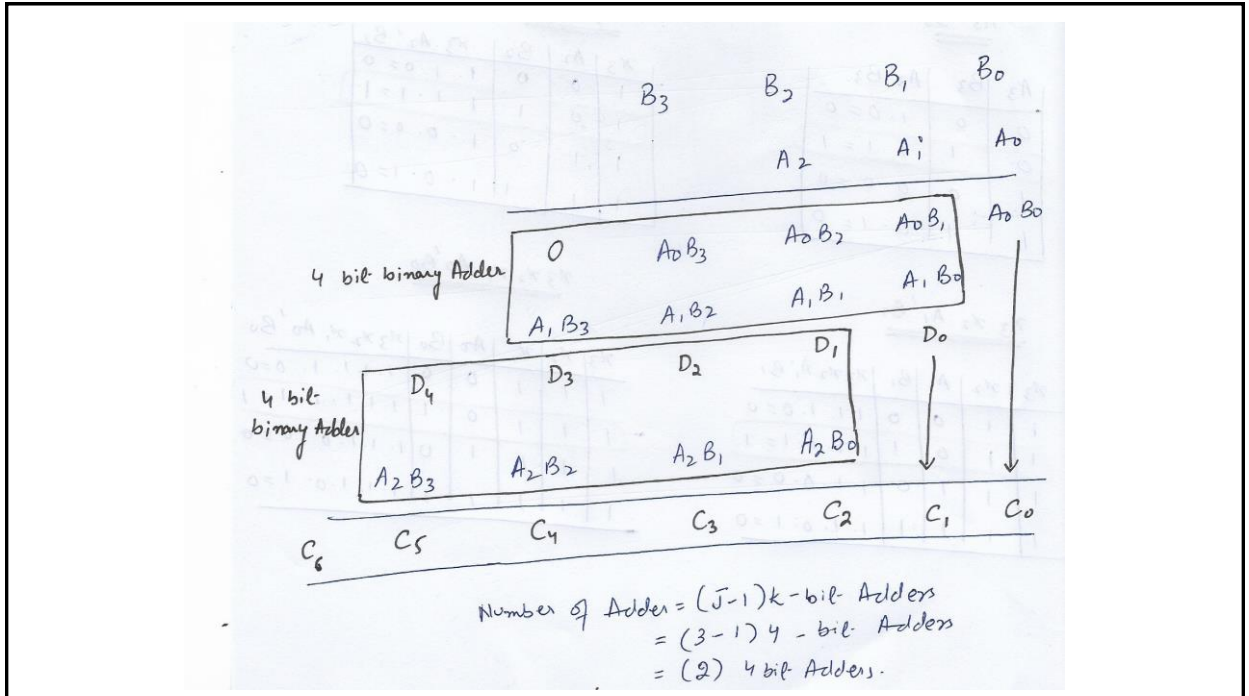

41

REFERENCES

- X Chapter 4 – Digital Design Morris Mano
- X Template is taken from slides carnival.



42