
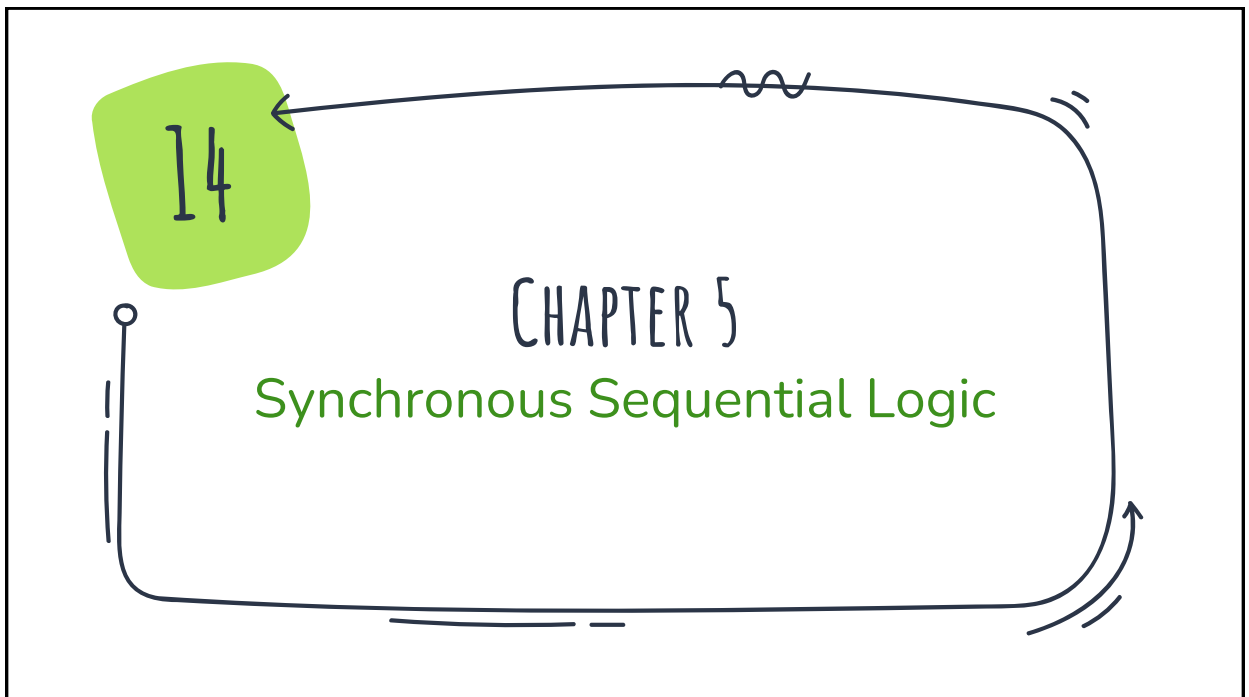


1

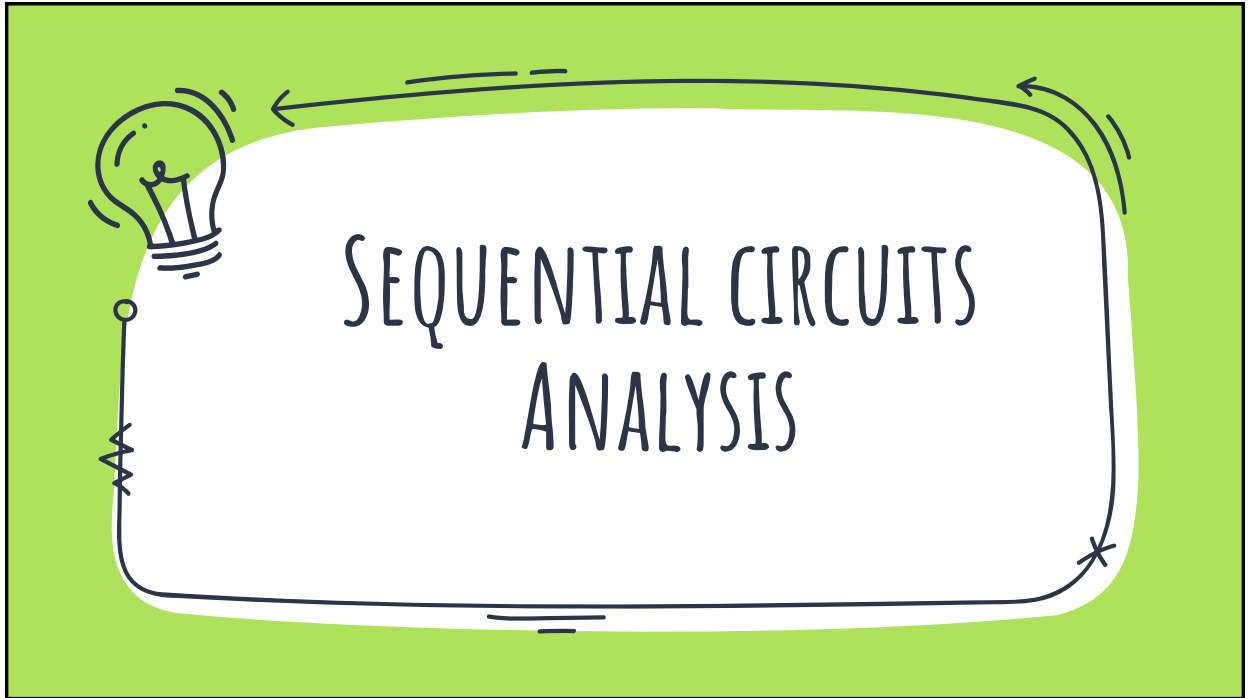

2




4

ANALYSIS OF SEQUENTIAL CIRCUITS

- X How to design machines that go through a sequence of events
- X Earlier we learned how to specify combinational circuits
 - X Truth tables, Boolean equations, ...
- X Now extend to synchronous sequential circuits
 - X Include time
 - X Use 'state tables' and 'state diagrams'

5

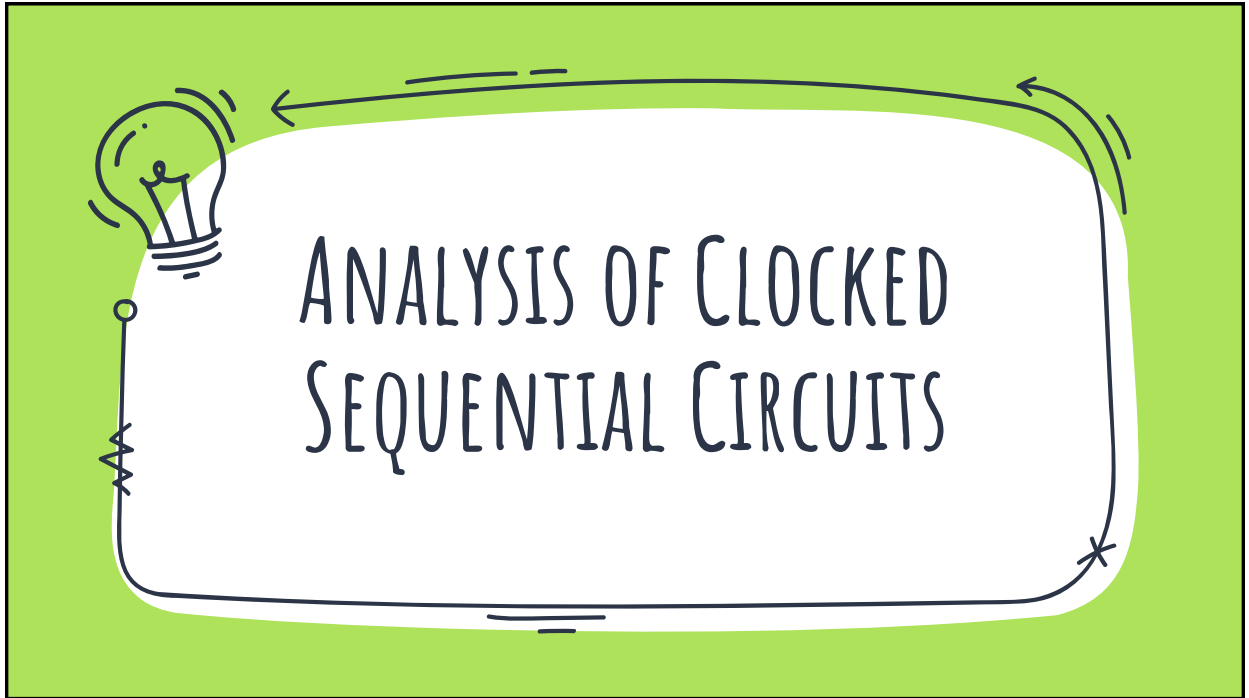

6

ANALYSIS OF CLOCKED SEQUENTIAL CIRCUITS

1. State/Output Equations (*transition/characteristic equation*)
 - Specifies the next state as a function of present state and input
2. State Table (*transition/characteristic table*)
 - Displays the relationship between various states in a table form
 - *Present State, Input, Next State, Output*
3. State Diagram
 - Graphic representation
 - States represented by circles
 - Lines represent transition




7

STATE TABLE

- X State Table
- X It is like truth table but with states added

8

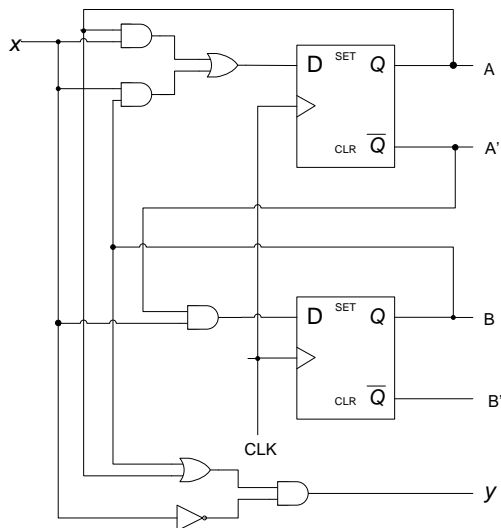

Since $A(t+1)=D$,
 $D=Ax+Bx$
 $A(t+1)=Ax+Bx$

$B(t+1)=D$, where $D=A'x$
 $B(t+1)=A'x$


And

$$y(t) = [A(t) + B(t)] x'(t)$$

$$y = (A + B)x'$$

Present State		Input	Next State		Output
A	B	x	A	B	y
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0

10

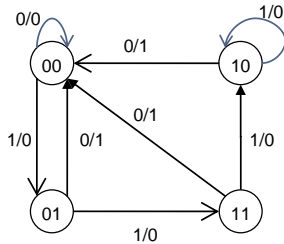

Since D input of the flip flop determines the next state, we can write a set of state equation as

$$A(t+1) = Ax + Bx$$

$$B(t+1) = A'x$$

And


$$y(t) = [A(t) + B(t)] x'(t)$$

$$y = (A + B)x'$$

Present State		Input x	Next State		Output y
A	B		A	B	
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	1	1	0	0
1	1	0	0	0	1
1	1	1	1	0	0


11

STATE DIAGRAM – MEALY MODEL

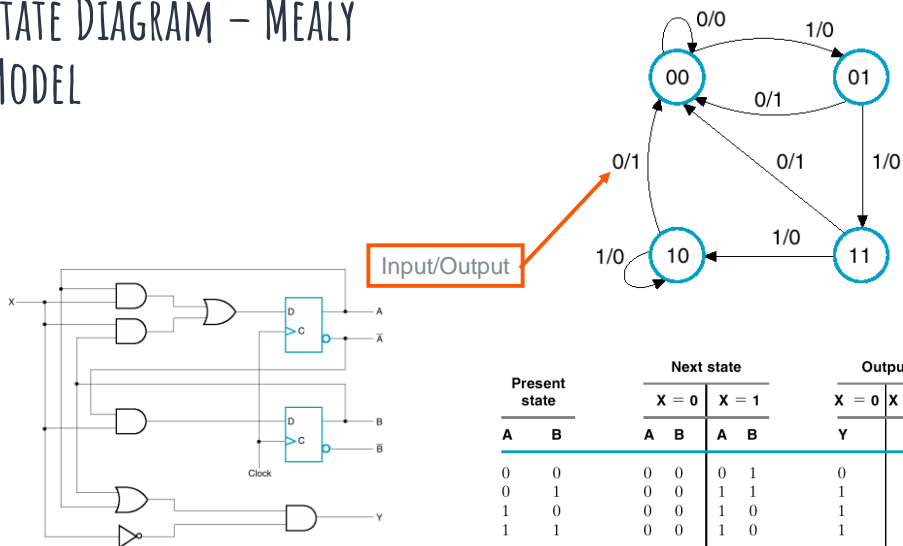


Present state		Next state				Output	
		X = 0		X = 1		X = 0	X = 1
A	B	A	B	A	B	Y	Y
0	0	0	0	0	1	0	0
0	1	0	0	1	1	1	0
1	0	0	0	1	0	1	0
1	1	0	0	1	0	1	0

12

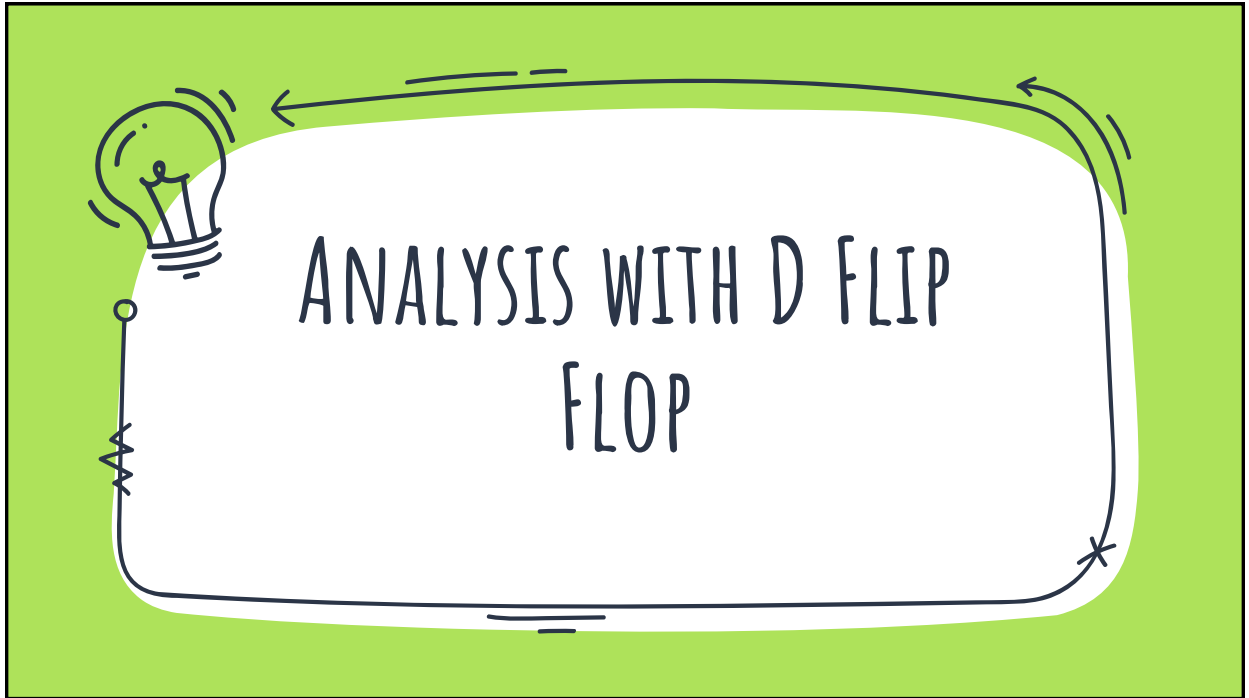

13

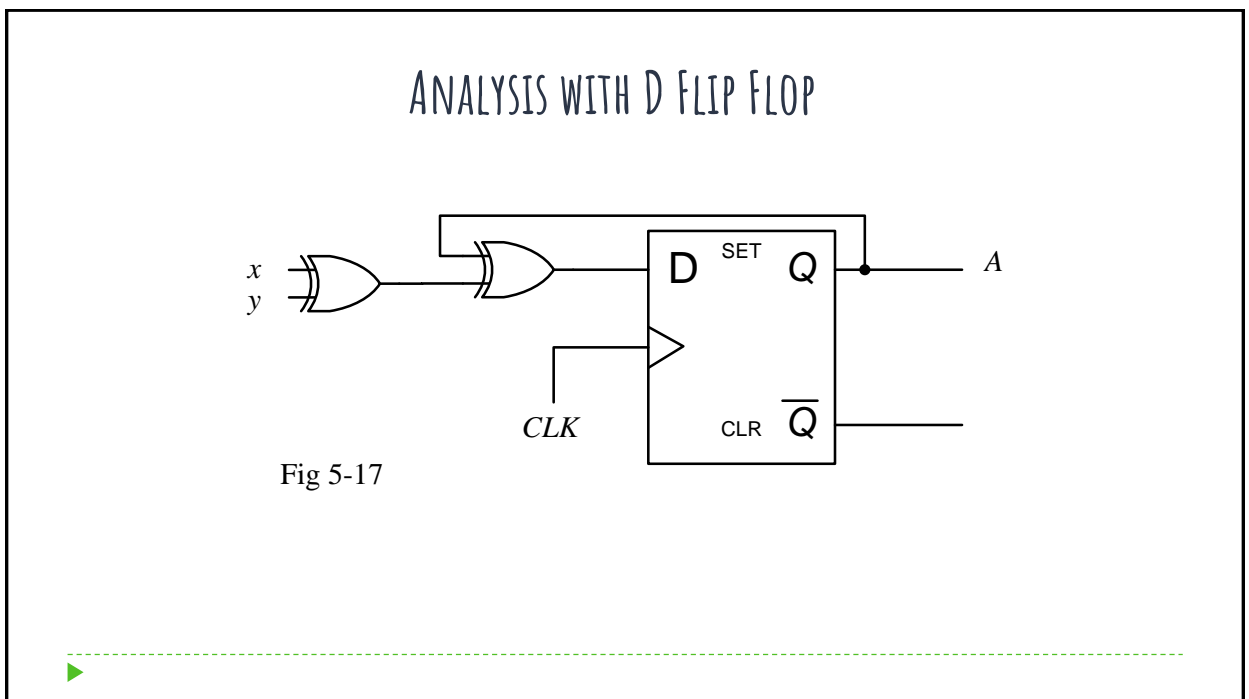

14

ANALYSIS WITH D FLIP FLOP

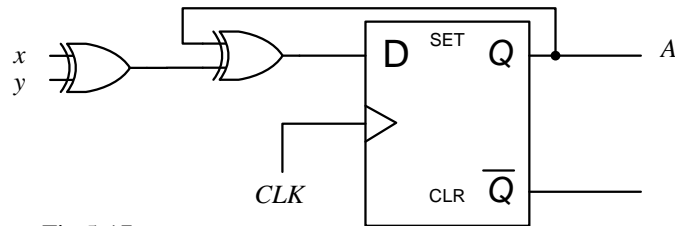


Fig 5-17

$\times A(t+1) = D_A$
 $\times D_A = A \oplus x \oplus y$
 $\times A(t+1) = A \oplus x \oplus y$



15

ANALYSIS WITH D FLIP FLOP

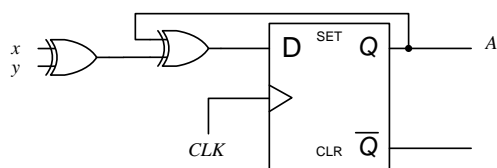



Fig 5-17

$\times A(t+1) = A \oplus x \oplus y$

Present State	Input		Next State
A	x	y	A
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1



16

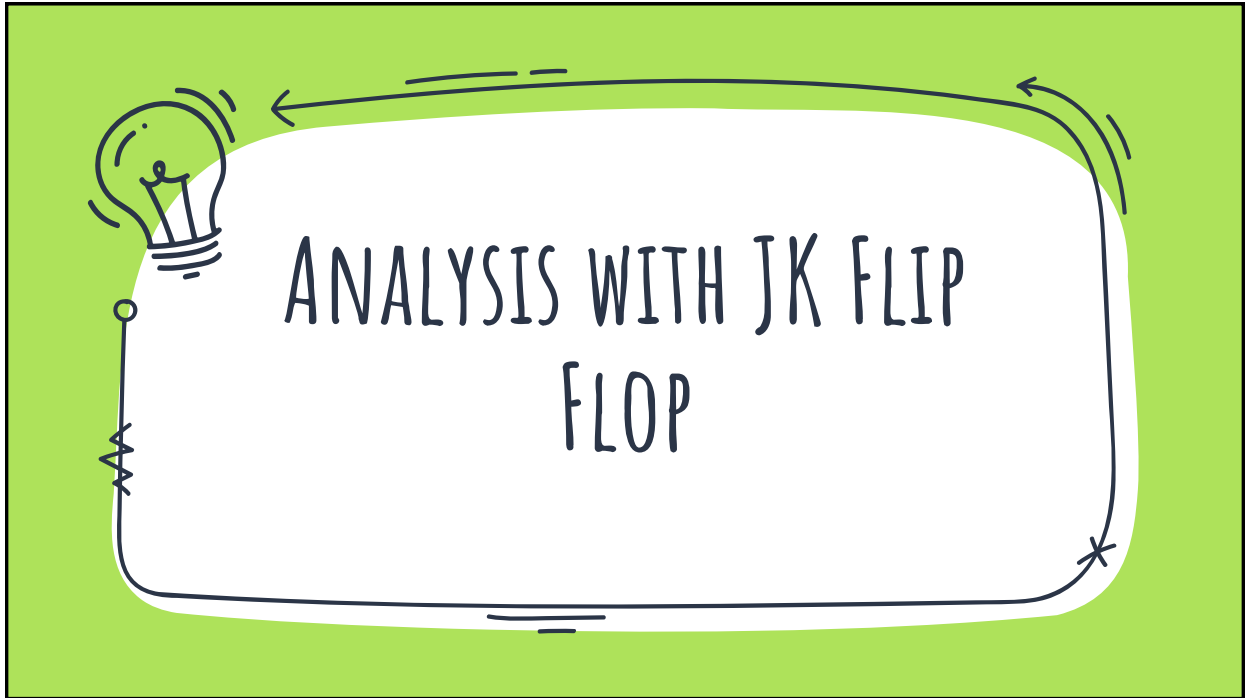

17

ANALYSIS PROCEDURE OF FLIP FLOP

X The next-state value of a sequential circuit that uses flip-flops can be derived using the following procedure.

1. determine the flip-flop input equation in terms of present state and input variable.
2. List the binary values of each input equation
3. Use the corresponding flip-flop characteristic table to determine the next values in the state table.



18

ANALYSIS WITH JK FLIP FLOP

$$Q(t+1) = JQ' + K'Q$$

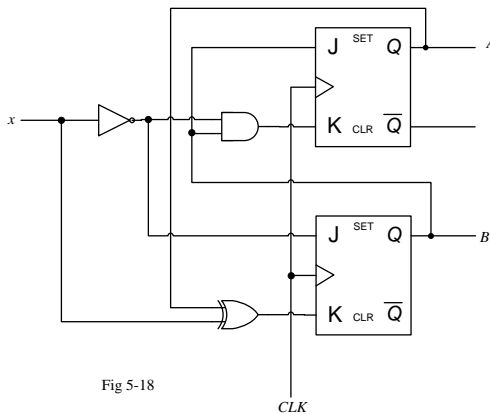


Fig 5-18

$$J_A = B$$

$$J_B = x'$$

$$K_A = Bx'$$

$$K_B = A'x + Ax'$$

$$= A \oplus x$$

$$A(t+1) = J_A A' + K_A' A$$

$$= A'B + (Bx')' A$$

$$= A'B + (B' + x) A$$

$$= A'B + AB' + Ax$$

$$B(t+1) = J_B B' + K_B' B$$

$$= B'x' + (A'x + Ax) B$$

$$= B'x' + ABx + A'Bx'$$

19

ANALYSIS WITH JK FLIP FLOP

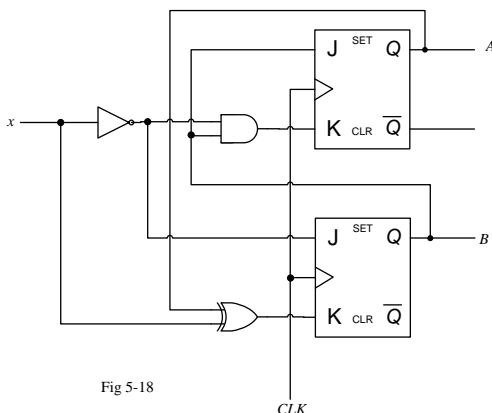


Fig 5-18

Present State		Input	Next State	
A	B		A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1

$$A(t+1) = J_A A' + K_A' A$$


$$= A'B + AB' + Ax$$

$$B(t+1) = J_B B' + K_B' B$$

$$= B'x' + ABx + A'Bx'$$

21

ANALYSIS WITH JK FLIP FLOP

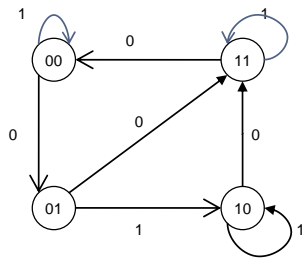

Present State		Input x	Next State	
A	B		A	B
0	0	0	0	1
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	1	1
1	0	1	1	0
1	1	0	0	0
1	1	1	1	1


22



24

ANALYSIS WITH T FLIP-FLOPS:


X Same procedure as J-K flip-flops.

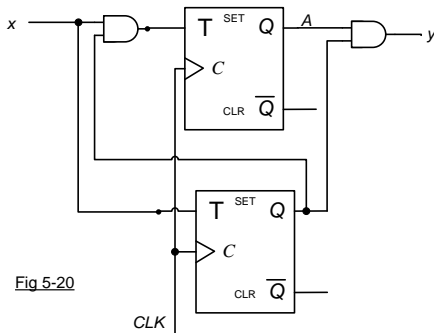

$$Q(t+1) = TQ' + T'Q$$

25

ANALYSIS WITH T FLIP-FLOPS:

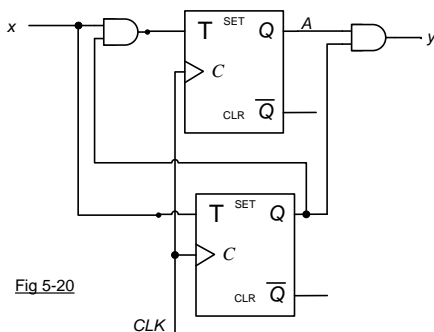


- X $Q(t+1) = T'Q + TQ'$
- X $A(t+1) = T_A'A + T_A A'$
- X $T_A = Bx,$
- X $A(t+1) = (Bx)'A + (Bx)A'$
- X $= (B' + x')A + (Bx)A'$
- X $= AB' + Ax' + A'Bx$
- X $T_B = X,$
- X $B(t+1) = T_B'B + T_B B' = T_B \oplus B$
- X $= x \oplus B$
- X $y = AB$

26

ANALYSIS WITH T FLIP-FLOPS:


X Same procedure as J-K flip-flops.

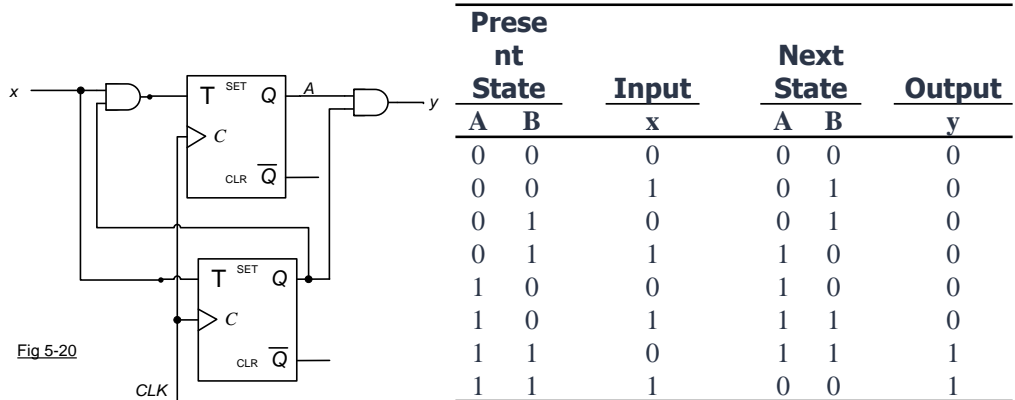

27

ANALYSIS WITH T FLIP-FLOPS:

X Same procedure as J-K flip-flops.

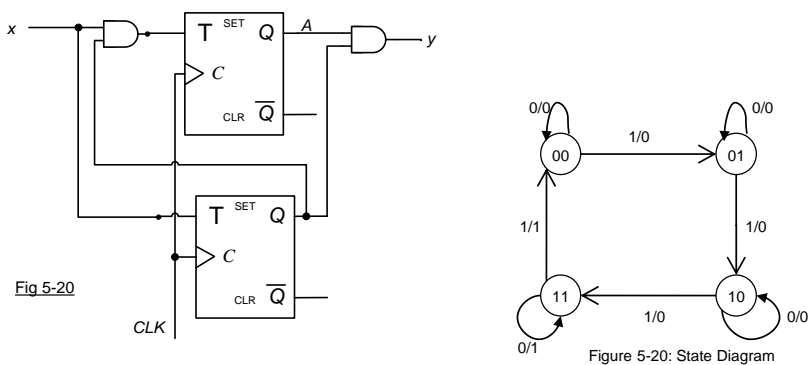

28



40

REFERENCES

- X Chapter 5 and 6 – Digital Design Morris Mano
- X Template is taken from slides carnival.

Slides Carnival

41