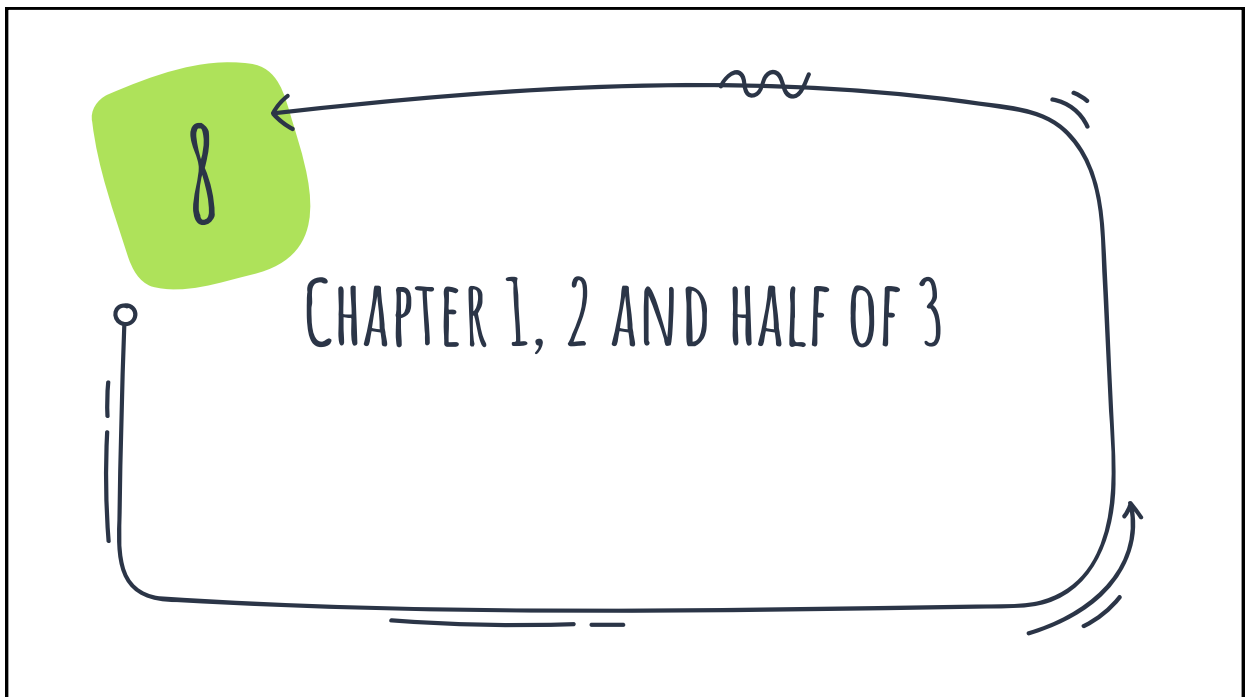



1




2



3

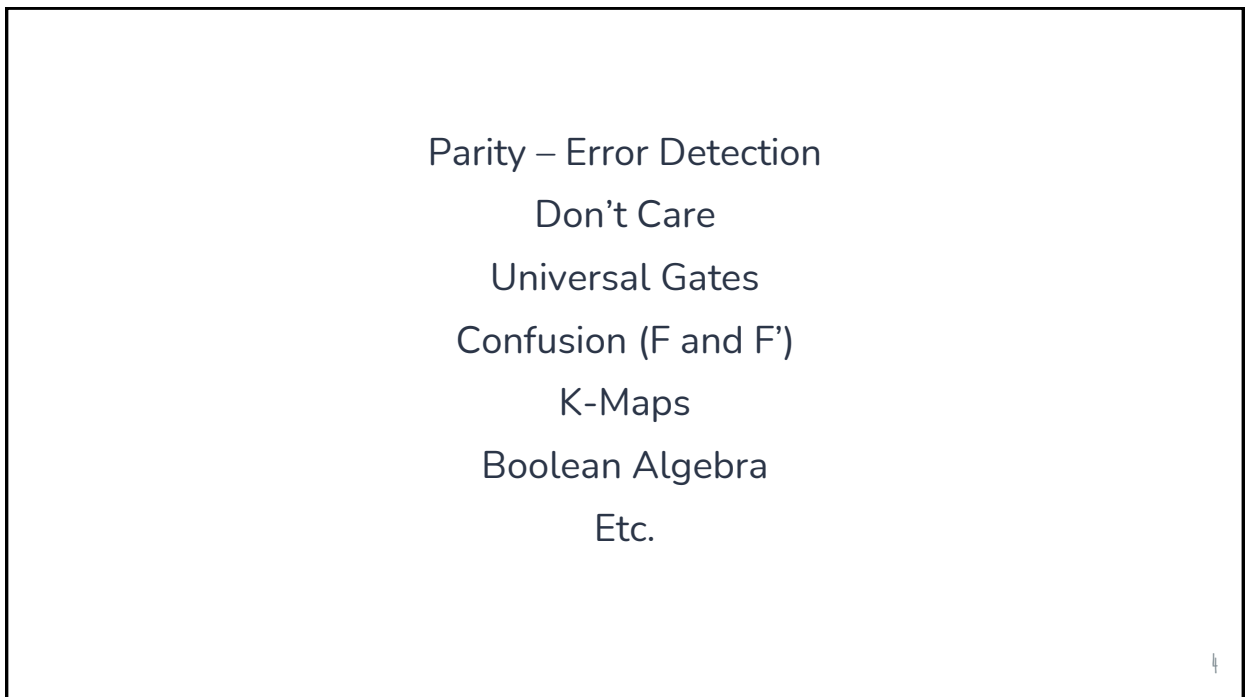


4

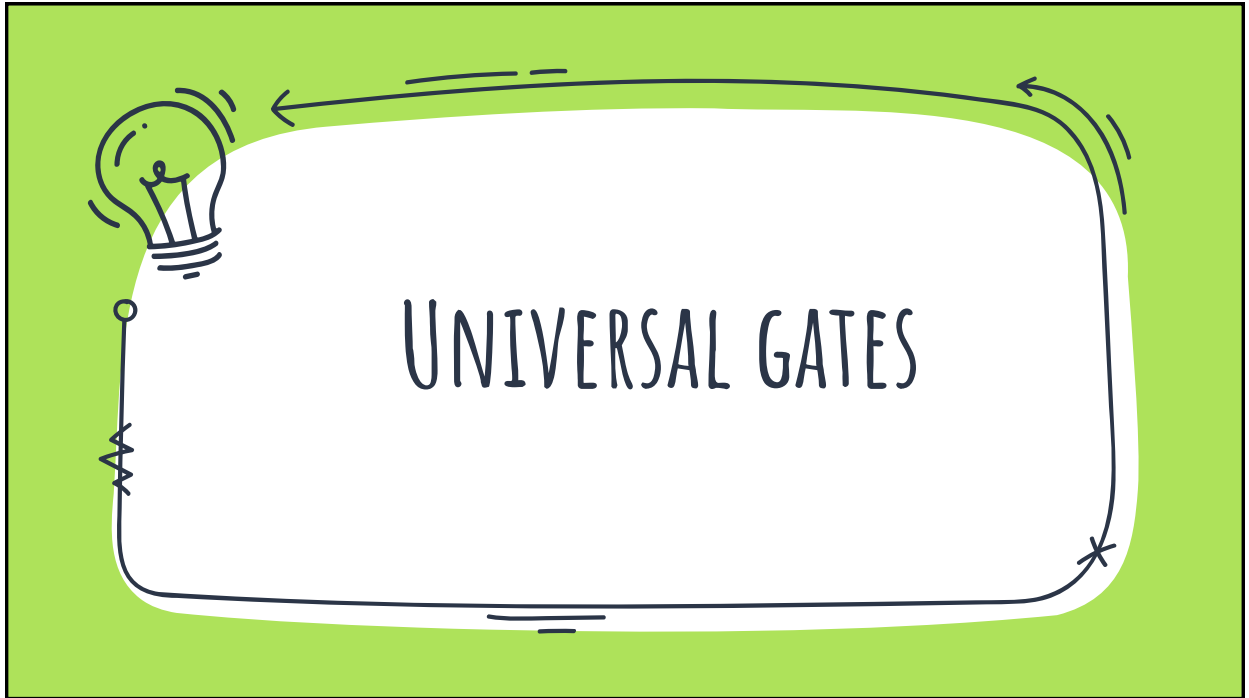

5

UNIVERSAL GATES

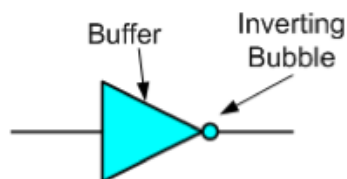- X NAND and NOR are universal gates.
- X Universal gate because they can be used to implement any logic gate
- X The small circle (bubble) at the output of the graphic symbol of a NOT gate is formally called a negation indicator and designates the logical complement.




6

NAND GATE

X Complement of AND

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

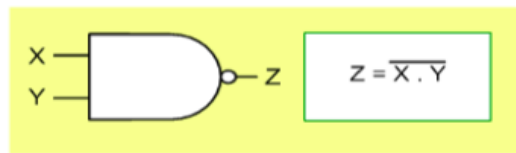


7

7

NOR GATE

X Complement of OR

X	Y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

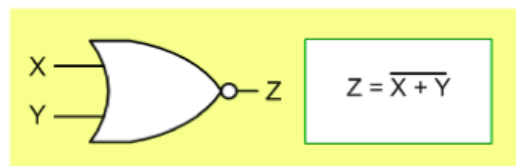

8

8

UNIVERSAL GATES

- X NAND and NOR gates are economical, easy to fabricate and used as the basic gates used in all IC digital logic families.
- X AND is implemented as an NAND gate followed by inverter (Not the other way Round)
- X OR is implemented as a NOR gate followed by inverter (Not the other way Round)

9

9

UNIVERSAL GATES


- X To prove that any Boolean function can be implemented using only NAND gates, it can be shown that the AND, OR, and NOT operations can be performed using only these gates.

10

10

INVERTER USING ONLY NAND GATE

X First Method

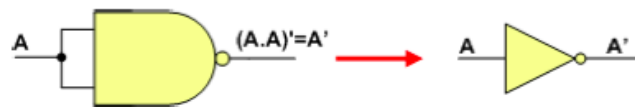


11

11

INVERTER USING ONLY NAND GATE

X Second method

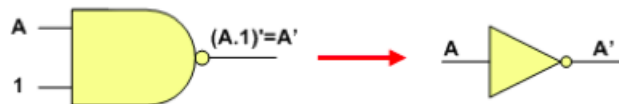


12

12

AND USING ONLY NAND GATES

X Using NAND as AND

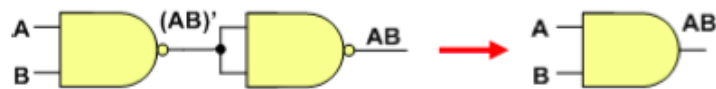


13

13

OR USING ONLY NAND GATES

X Using NAND implementing equivalent OR

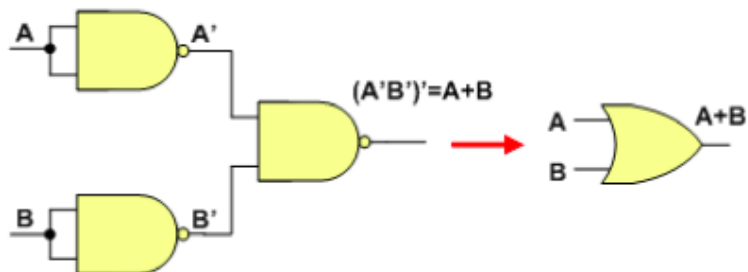

X Thus, the NAND gate is a universal gate since it can implement the AND, OR and NOT functions.

14

14

NOT, AND, OR USING NOR


- X To prove that any Boolean function can be implemented using only NOR gates, it can be shown that the AND, OR, and NOT operations can be performed using only these gates.

15

15

INVERTER USING ONLY NOR GATE


- X First Method:

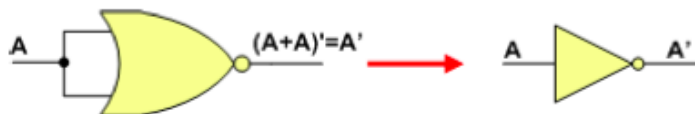

16

INVERTER USING ONLY NOR GATE

X Second Method

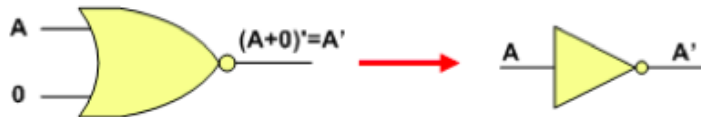

17

17


OR USING ONLY NOR GATES



18

18

AND USING ONLY NOR GATES

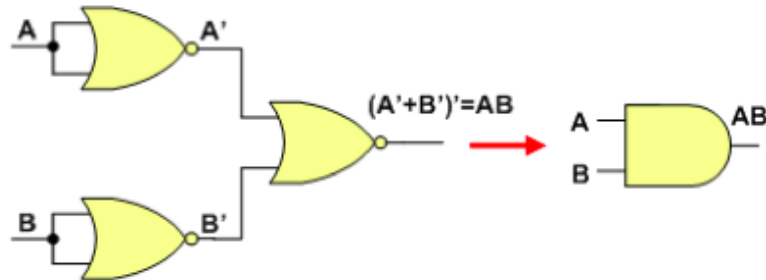


- ✕ Thus, the NOR gate is a universal gate since it can implement the AND, OR and NOT functions.

19

19

EQUIVALENT GATES - SUMMARY

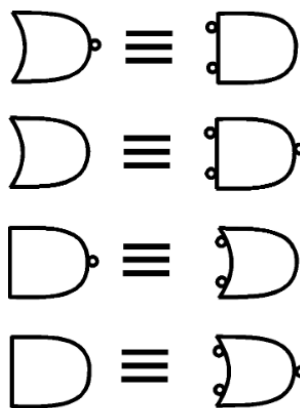

AND Gate and OR Gate Equivalents




20

20

EQUIVALENT GATES (1)

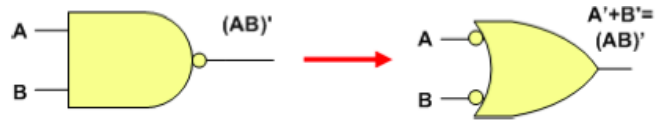- Some important cases of gate equivalence
- A NAND gate is equivalent to an inverted-input OR gate.



21

21

NAND GATE



AND-Invert

$$F = (xyz)'$$




Invert-OR

$$F = x' + y' + z'$$


22

EQUIVALENT GATES (2)

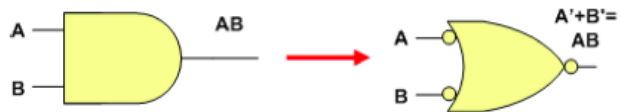An **AND** gate is equivalent to an **inverted-input NOR** gate.



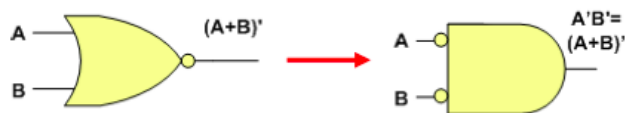A **NOR** gate is equivalent to an **inverted-input AND** gate.



23

23

NOR GATE



OR-Invert

$$F = (x+y+z)'$$



Invert-AND

$$F = x'y'z'$$

24

EQUIVALENT GATES (3)

An **OR** gate is equivalent to an **inverted-input NAND** gate.



Two **NOT** gates in series are same as a **buffer** because they cancel each other as $A'' = A$.



25

25

NOT GATE



AND-Invert



OR-Invert



Buffer-Invert



26

TWO-LEVEL IMPLEMENTATIONS - RECALL

- X Boolean functions in either SOP or POS forms can be implemented using 2-Level implementations.
- X For SOP forms AND gates will be in the first level and a single OR gate will be in the second level.
- X For POS forms OR gates will be in the first level and a single AND gate will be in the second level.
- X **Note that using inverters to complement input variables is not counted as a level.**

27

27

TWO-LEVEL IMPLEMENTATIONS

- X SOP forms can be implemented using only NAND gates, while POS forms can be implemented using only NOR gates.

Example 1: Implement the following SOP function using only universal gates.

$$F = XZ + Y'Z + X'YZ$$


- X Being an SOP expression, it is implemented in 2-levels as shown in the figure.

28

28

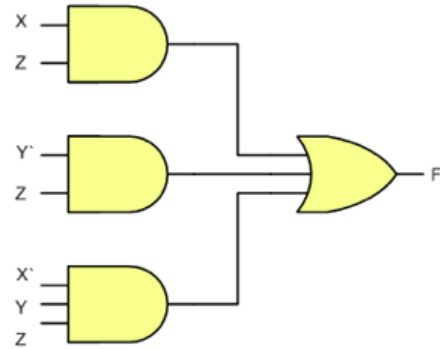EXAMPLE 1

- X SOP \rightarrow NAND
- X $F = XZ + Y'Z + X'YZ$
- X First implement with AND/OR
- X should have only two-levels.




29

29

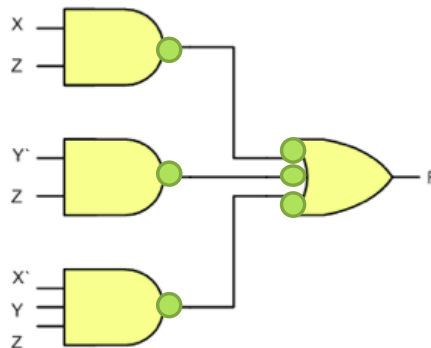EXAMPLE 1


- X For NAND:
- X Put bubbles at input of OR and output of AND



30

30

EXAMPLE 1

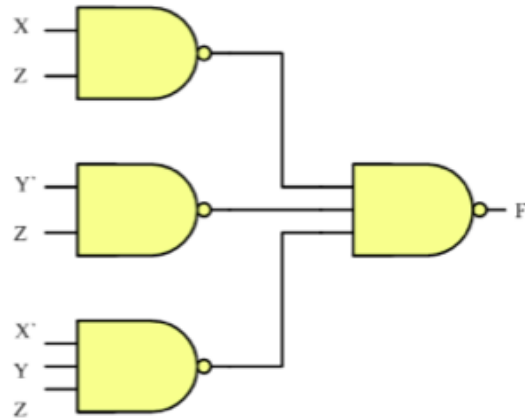

31

31

EXAMPLE 2

- Implement the following POS function

$$F = (X+Z) (Y'+Z) (X'+Y+Z)$$


- It should be implemented in 2-levels
- POS \rightarrow NOR

32

32

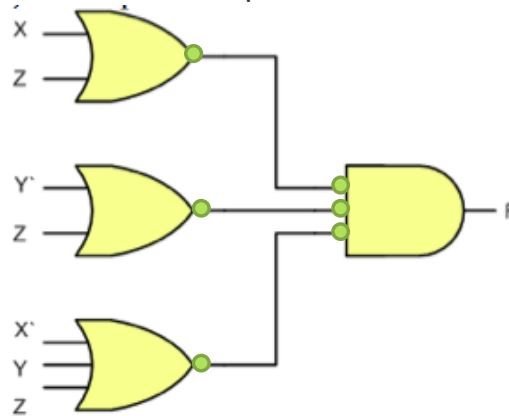EXAMPLE 2


- X Do it your self !
- X For NOR: Output of OR and input of AND



33

33

ANSWER!!!

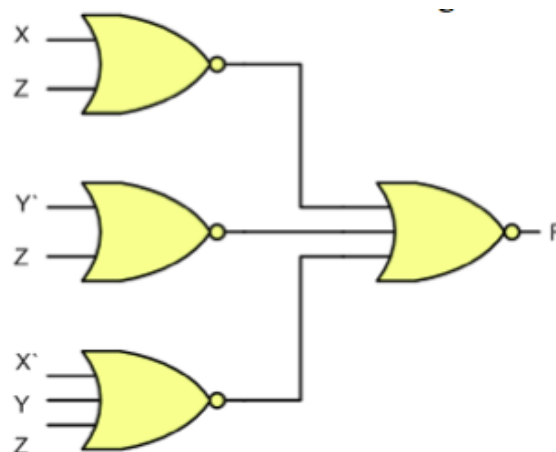


34


34

TWO-LEVEL NAND IMPLEMENTATION - EXAMPLE


$$F = AB + CD$$

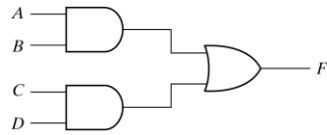

(a)

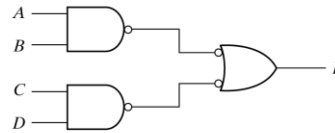

(b)

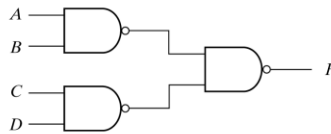

(c)


Three ways to implement $F = AB + CD$

35


TWO-LEVEL NAND IMPLEMENTATION - EXAMPLE

$$F(x, y, z) = \sum(1, 2, 3, 4, 5, 7)$$


$$F(x, y, z) = xy' + x'y + z$$

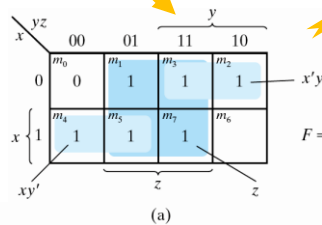

(a)

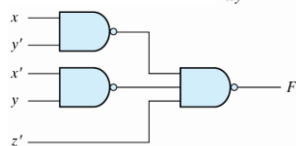


(c)

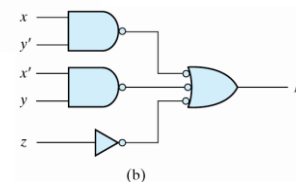


(b)

36

MULTILEVEL CIRCUITS – CONVERT TO NAND


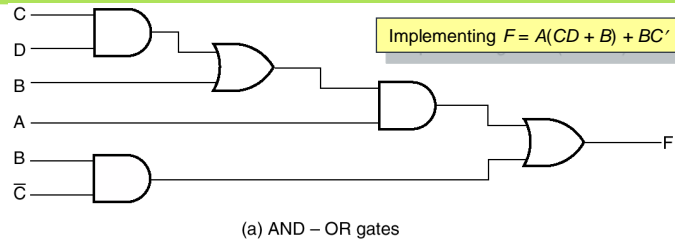


Note this complement

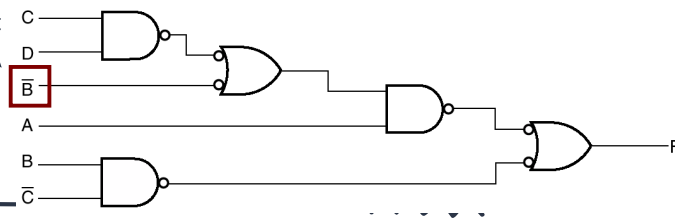

37

MULTILEVEL CIRCUITS – CONVERT TO NAND

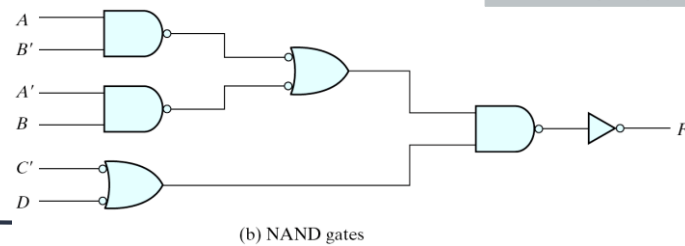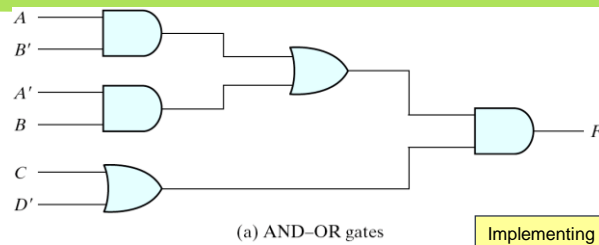


38

TWO-LEVEL NOR IMPLEMENTATION - CONVERT

X Implement and convert

Implementing $F = (A + B)(C + D)E$

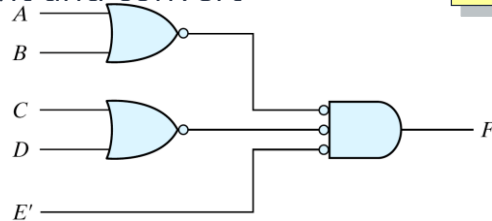


39

MULTILEVEL NOR CIRCUIT

Implementing $F = (AB' + A'B)(C + D')$

X Implement and Convert

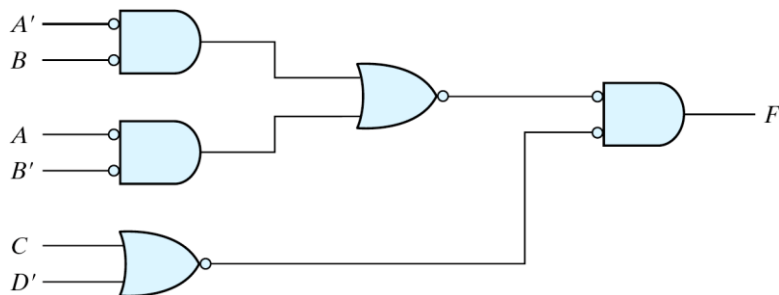

40