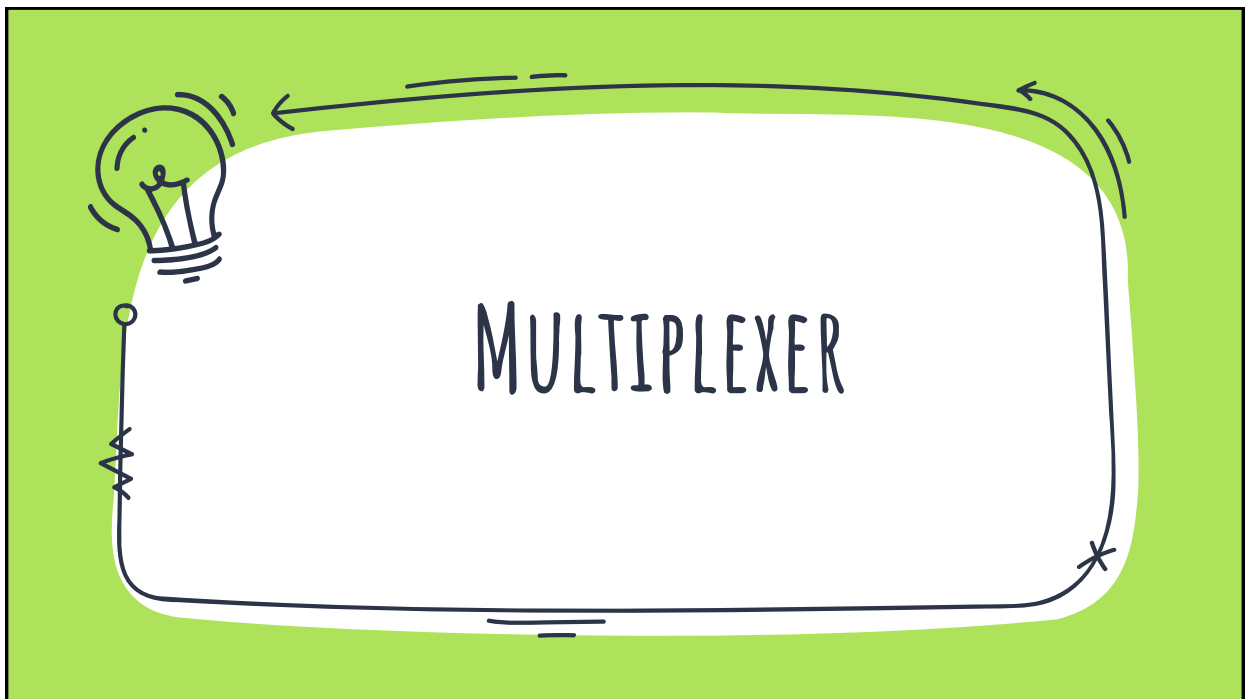


1



4


MULTIPLEXER

A multiplexer (MUX) selects one of multiple input signals and passes it to the output.

5

5


MULTIPLEXER

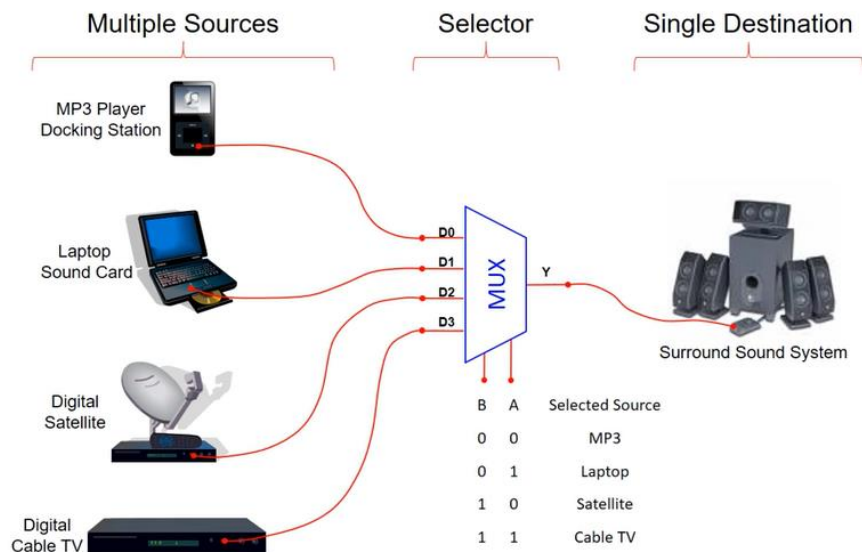


6

6

DEMULTIPLEXER

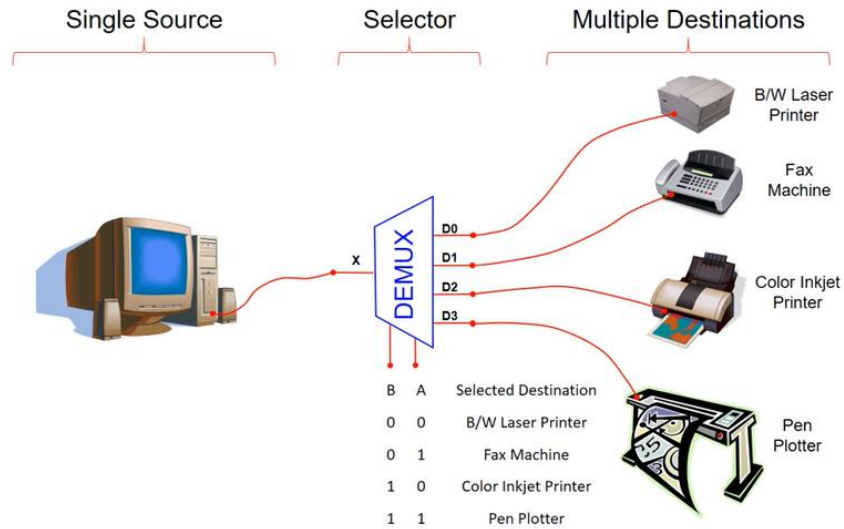


7

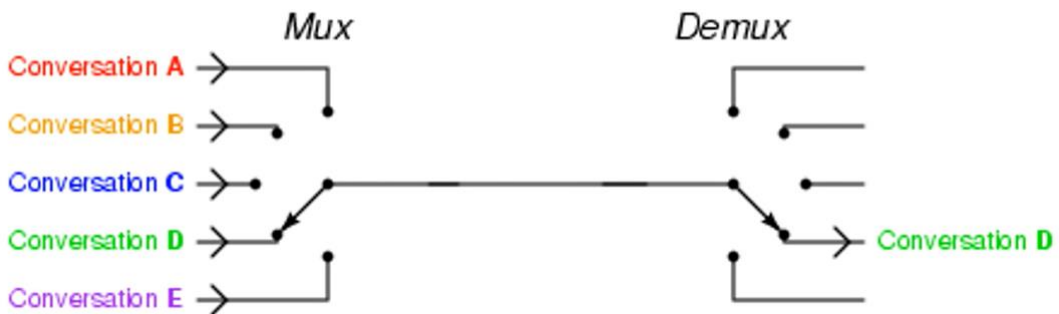

The basic function of a multiplexer: combining multiple inputs into a single data stream. On the receiving side, a demultiplexer splits the single data stream into the original multiple signals.

8


8

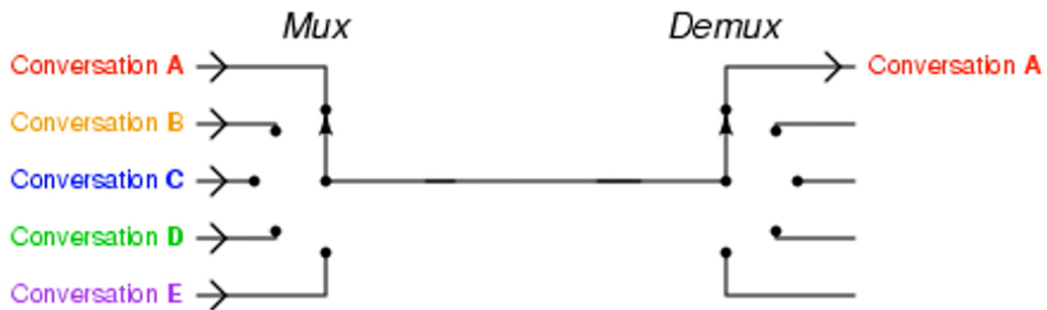

The basic function of a multiplexer: combining multiple inputs into a single data stream. On the receiving side, a demultiplexer splits the single data stream into the original multiple signals.

9


9

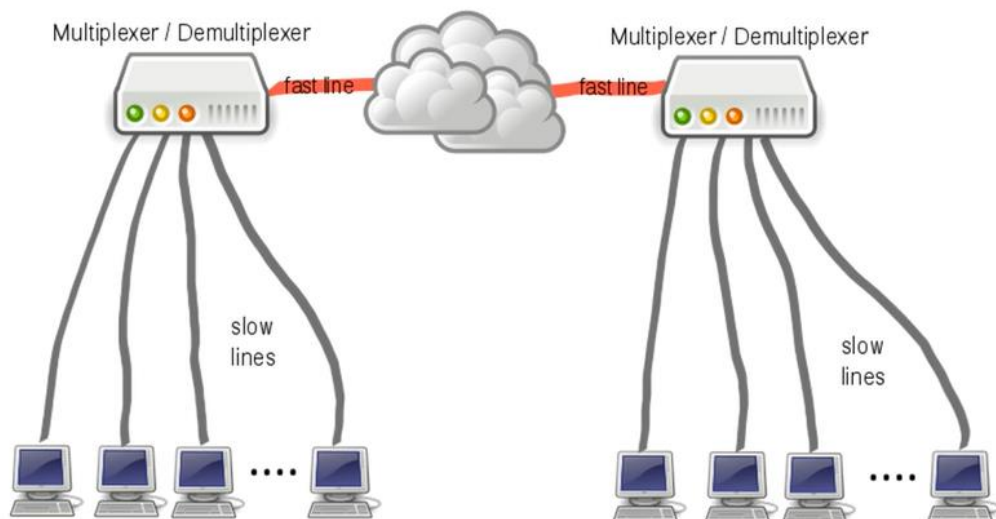

10

10


4-to-1 Multiplexer (MUX)

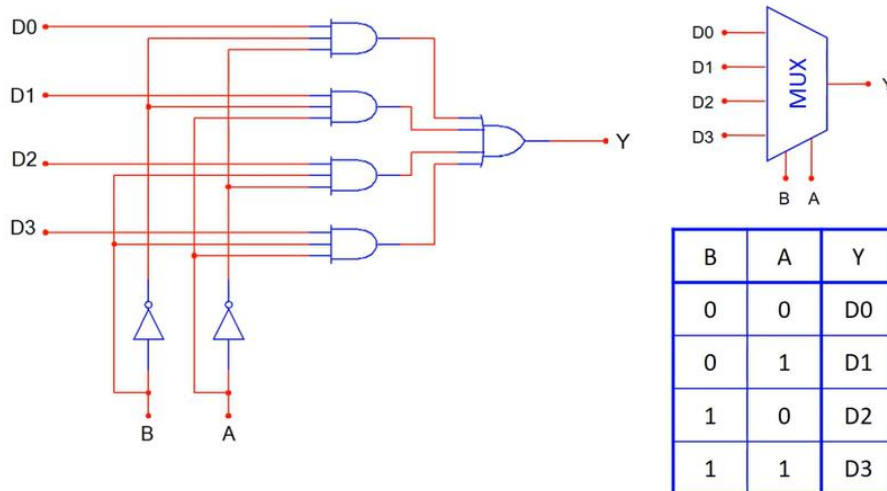

11

11


1-to-4 De-Multiplexer (DEMUX)

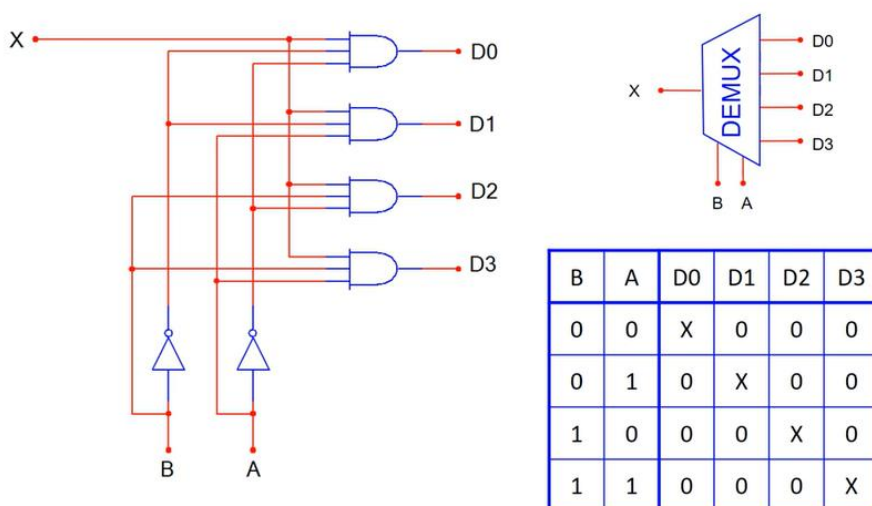

12

12


Medium Scale Integration MUX

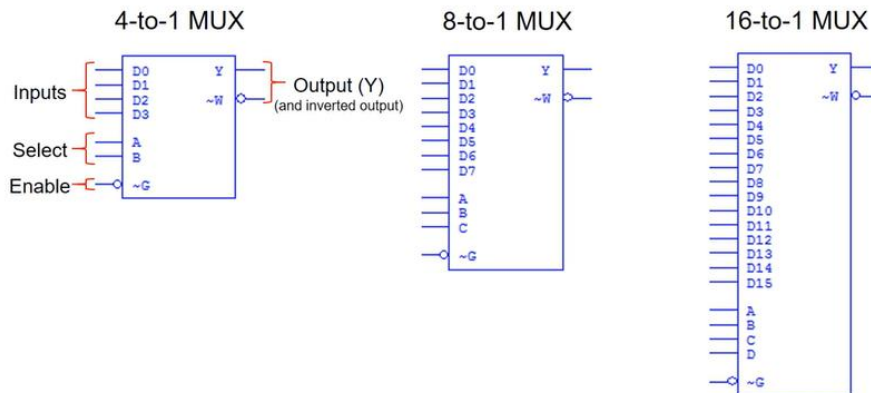

13

13

Medium Scale Integration DEMUX

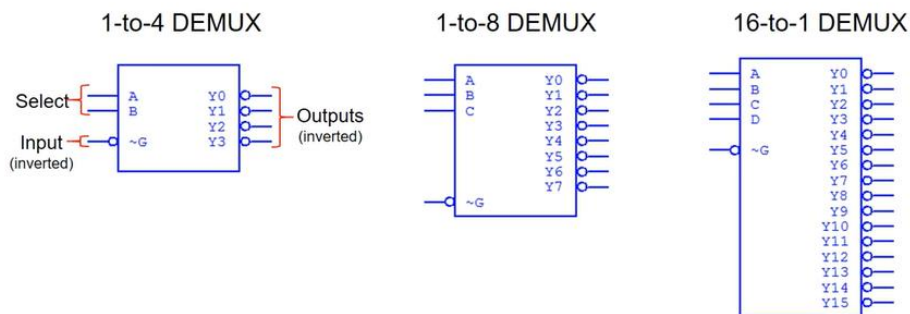


Note : Most Medium Scale Integrated (MSI) DEMUXs , like the three shown, have outputs that are inverted. This is done because it requires few logic gates to implement DEMUXs with inverted outputs rather than no-inverted outputs.

14

14

MULTIPLEXER (DATA SELECTOR)

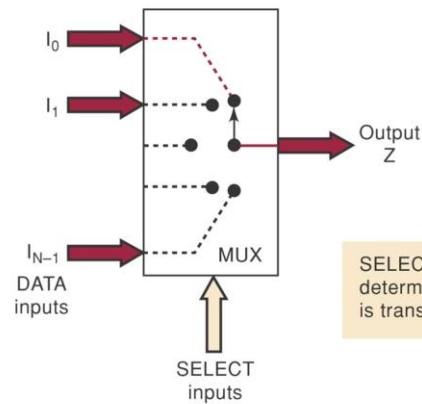- X Selects one of a set of inputs to pass on to output
- X Binary control code, n lines - Choose from 2^n inputs




SELECT input code determines which input is transmitted to output Z.

15

15


2-TO-1 LINE MUX

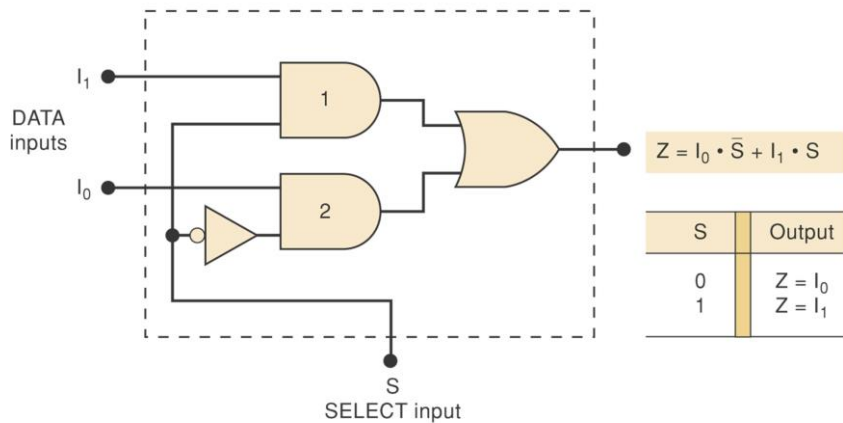

16

16


2-TO-1 LINE MUX

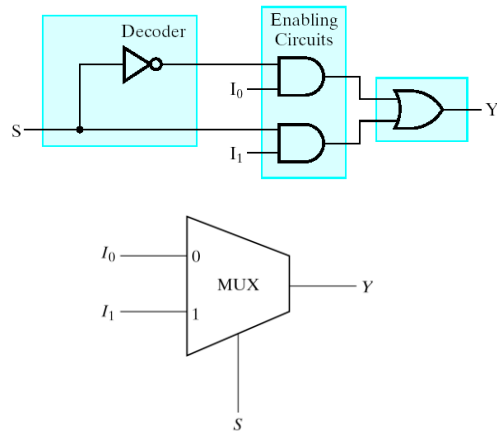

17

17


4-TO-1 LINE MUX

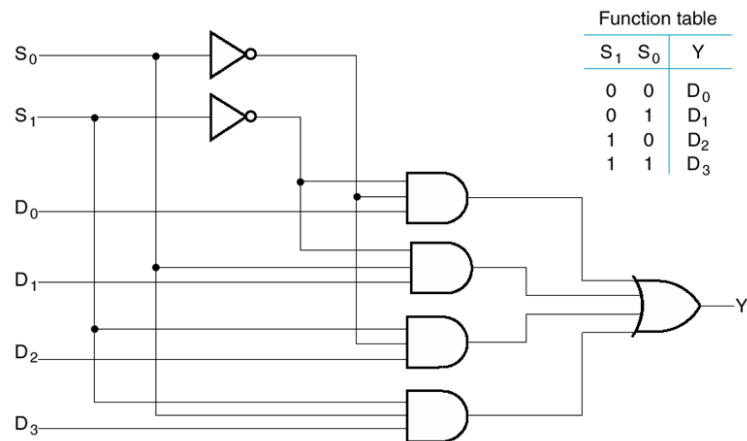

18

18

4-TO-1 LINE MUX

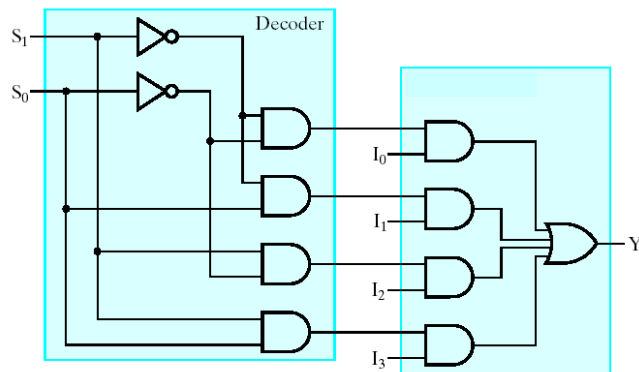


19

19

BOOLEAN FUNCTION IMPLEMENTATION

- Although the circuit contains four 2-to-1-line multiplexers, we are more likely to view it as a circuit that selects one of two 4-bit sets of data lines.
- As shown in the function table, the unit is enabled when $E = 0$.
- Then, if $S = 0$, the four A inputs have a path to the four outputs.
- If, by contrast, $S = 1$, the four B inputs are applied to the outputs.
- The outputs have all 0's when $E = 1$, regardless of the value of S .

160 Chapter 4 Combinational Logic

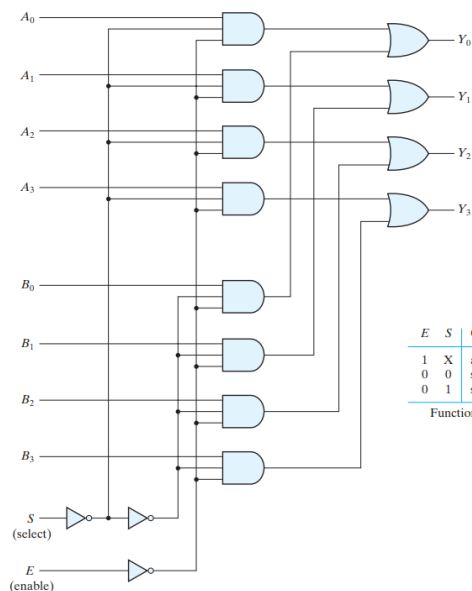


E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B

Function table

FIGURE 4.26
Quadrate two-to-one-line multiplexer

20

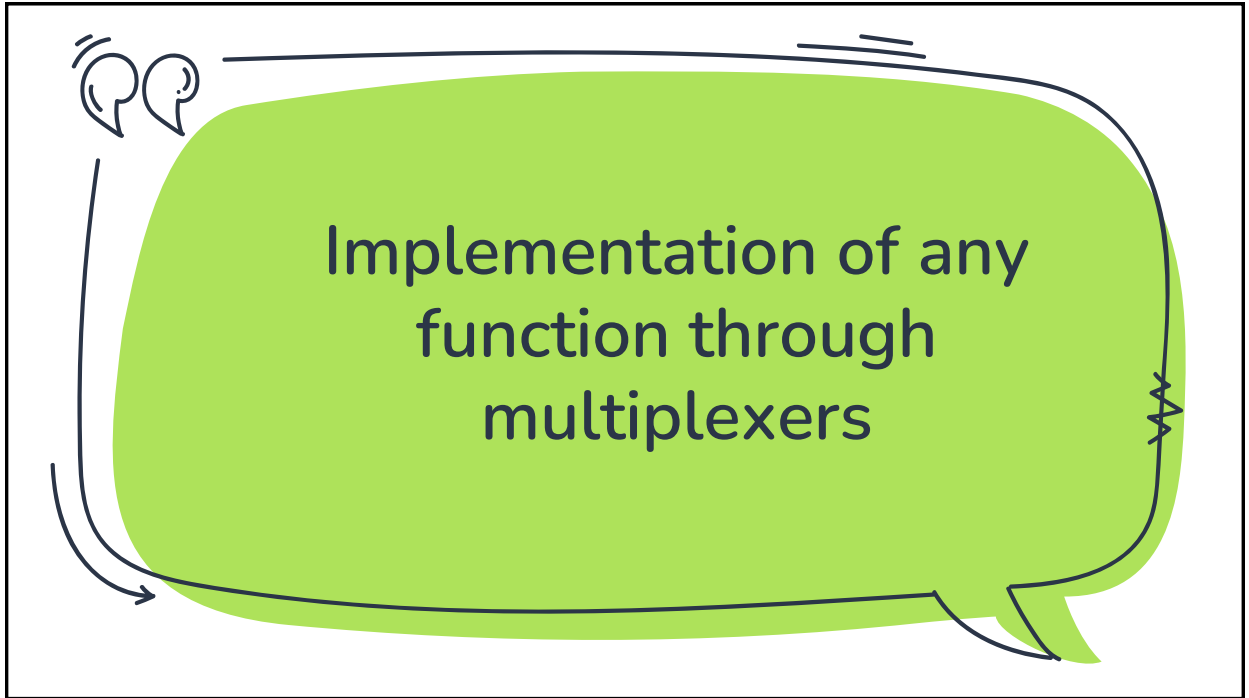


21

Implementation of any function through Multiplexer

Truth Table $F(A, B, C) = \sum m(0, 2, 3, 7)$

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

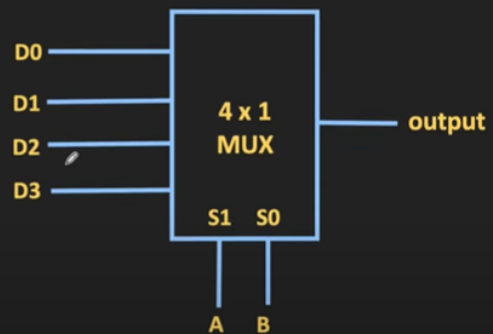


22

Example 1:

$$F(A, B, C) = \sum m(0, 2, 3, 7)$$

Truth Table

A	B	C	F	
0	0	0	1	
0	0	1	0	
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	0	
1	1	0	0	
1	1	1	1	

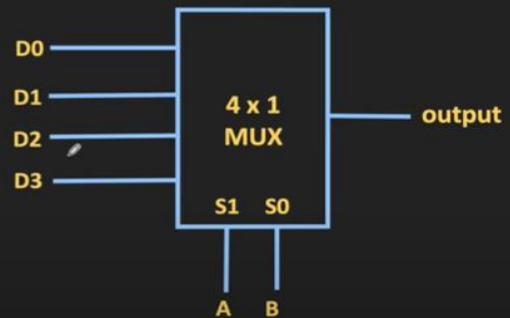


23

Example 1:

$$F(A, B, C) = \sum m(0, 2, 3, 7)$$

Truth Table

A	B	C	F	
0	0	0	1	$F = C'$
0	0	1	0	
0	1	0	1	$F = 1$
0	1	1	1	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	0	$F = C$
1	1	1	1	

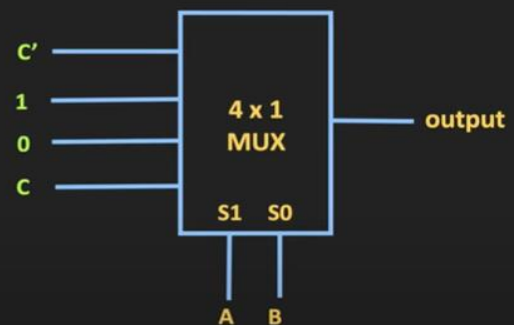


24

Example 2:

A	B	C	D	F	
0	0	0	0	0	
0	0	0	1	1	
0	0	1	0	0	
0	0	1	1	1	
0	1	0	0	0	
0	1	0	1	0	
0	1	1	0	1	
0	1	1	1	0	
1	0	0	0	0	
1	0	0	1	1	
1	0	1	0	0	
1	0	1	1	0	
1	1	0	0	1	
1	1	0	1	0	
1	1	1	0	1	
1	1	1	1	1	
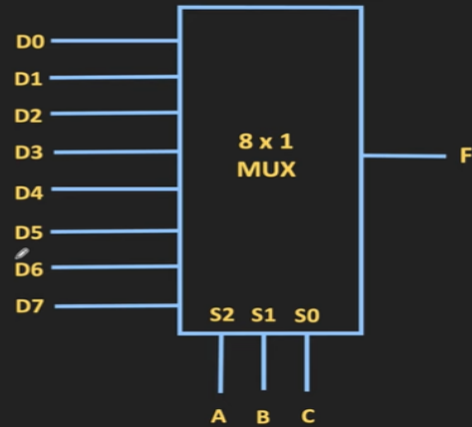
$$F(A, B, C, D) = \sum m(1, 3, 6, 9, 12, 14, 15)$$




25

Example 2:

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	$F = D$
0	0	1	0	0	$F = 0$
0	0	1	1	1	$F = D$
0	1	0	0	0	$F = 0$
0	1	0	1	0	$F = D'$
0	1	1	0	1	$F = D$
0	1	1	1	0	$F = 0$
1	0	0	0	0	$F = D$
1	0	0	1	1	$F = 0$
1	0	1	0	0	$F = D'$
1	0	1	1	0	$F = 0$
1	1	0	0	1	$F = D$
1	1	0	1	0	$F = D'$
1	1	1	0	1	$F = 1$
1	1	1	1	1	$F = 1$
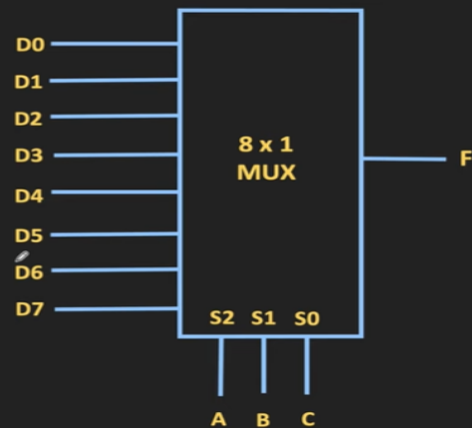
$$F(A, B, C, D) = \sum m(1, 3, 6, 9, 12, 14, 15)$$



26

Example 3:

Implementation of any function through Mux.

$$F(A, B, C) = \sum m(0, 2, 3, 7)$$

Step 1: $n=3$, $n-1=2$ Selection
 $2^{n-1} \times 1 = 4 \times 1$ mux

Step 2:


A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

$$F = C'$$

$$F = 1$$

$$F = 0$$

$$F = C$$

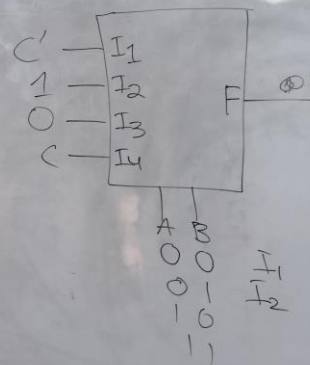

27

Example 4:

Implementation of any function through Mux.

$$F(A, B, C, D) = \sum m(0, 2, 6, 10, 11, 12, 15)$$

Step 1: $n=4$, $n-1=3$ Selection vars, $2^{n-1} \times 1 = 8 \times 1$ mux

Step 2:

A	B	C	D	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$F = D'$$

$$F = 0$$

$$F = D'$$


$$F = 0$$

$$F = D'$$

$$F = 0$$

$$F = D'$$

$$F = D$$

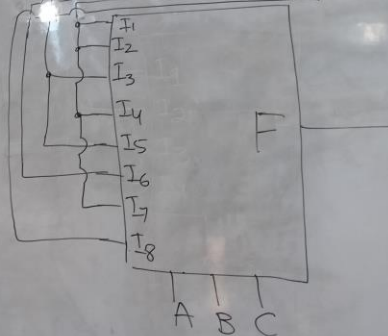


28

Implementation of any function through Multiplexer

Activity: Solve it yourself


A	B	C	F	
0	0	0	0	
0	0	1	1	
0	1	0	1	
0	1	1	1	
1	0	0	0	
1	0	1	0	
1	1	0	1	
1	1	1	0	

29

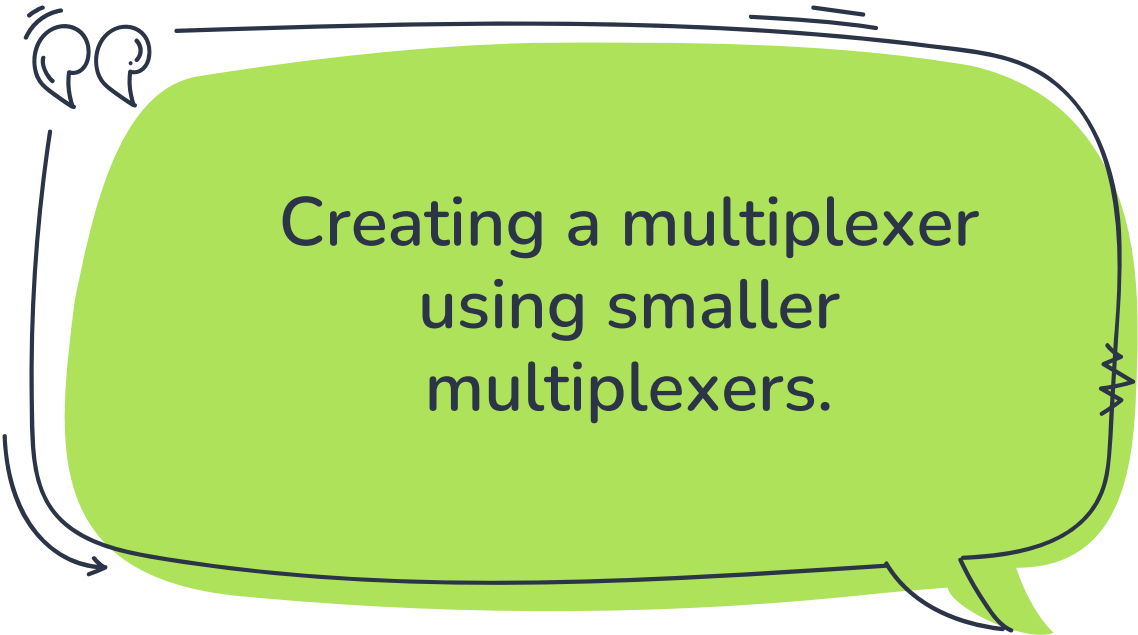


Creating a multiplexer
using smaller
multiplexers.


30

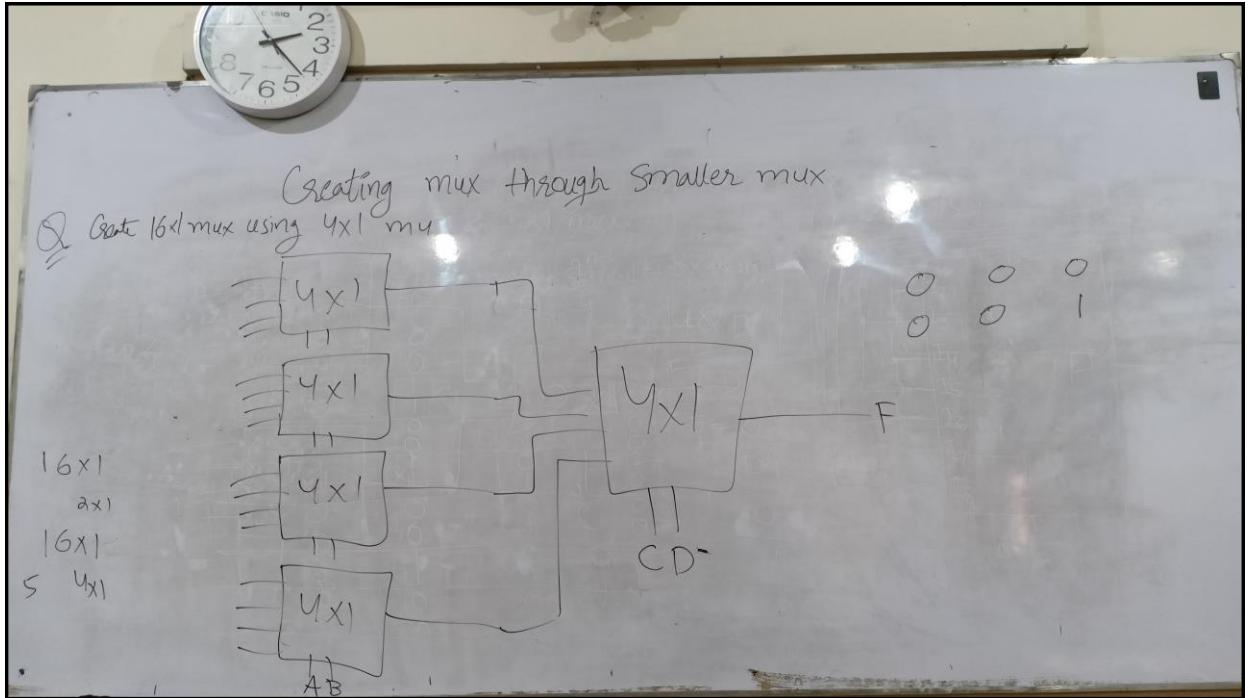


31

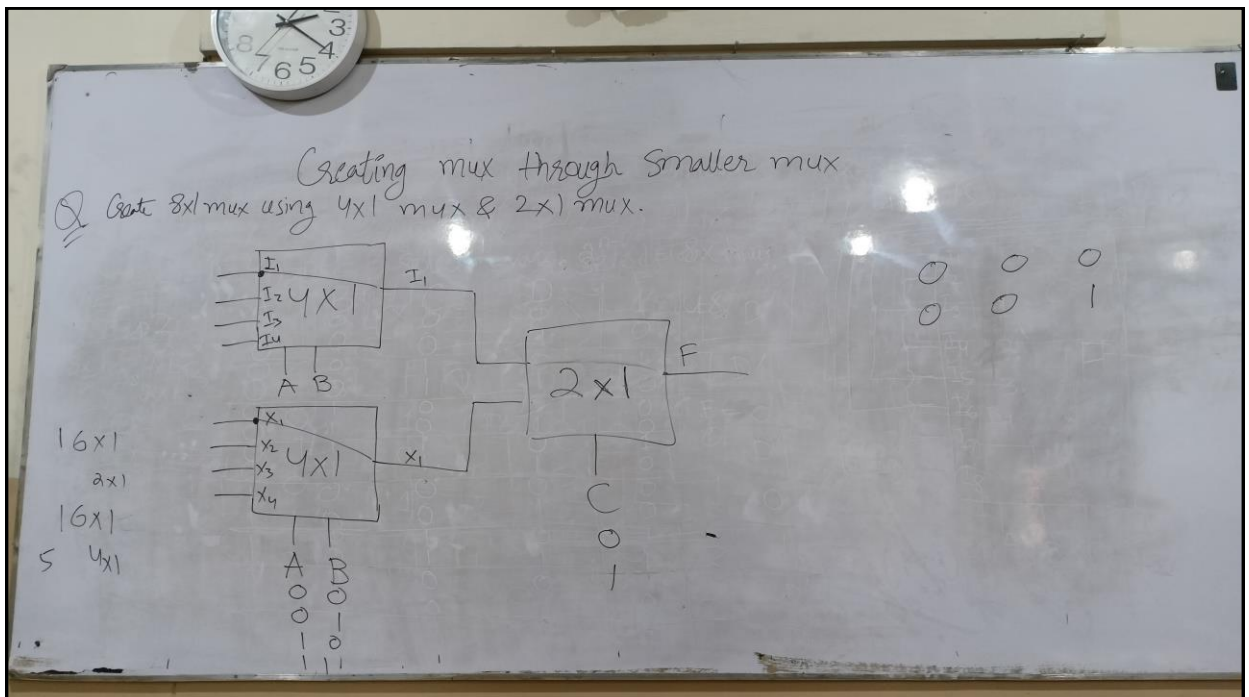

32

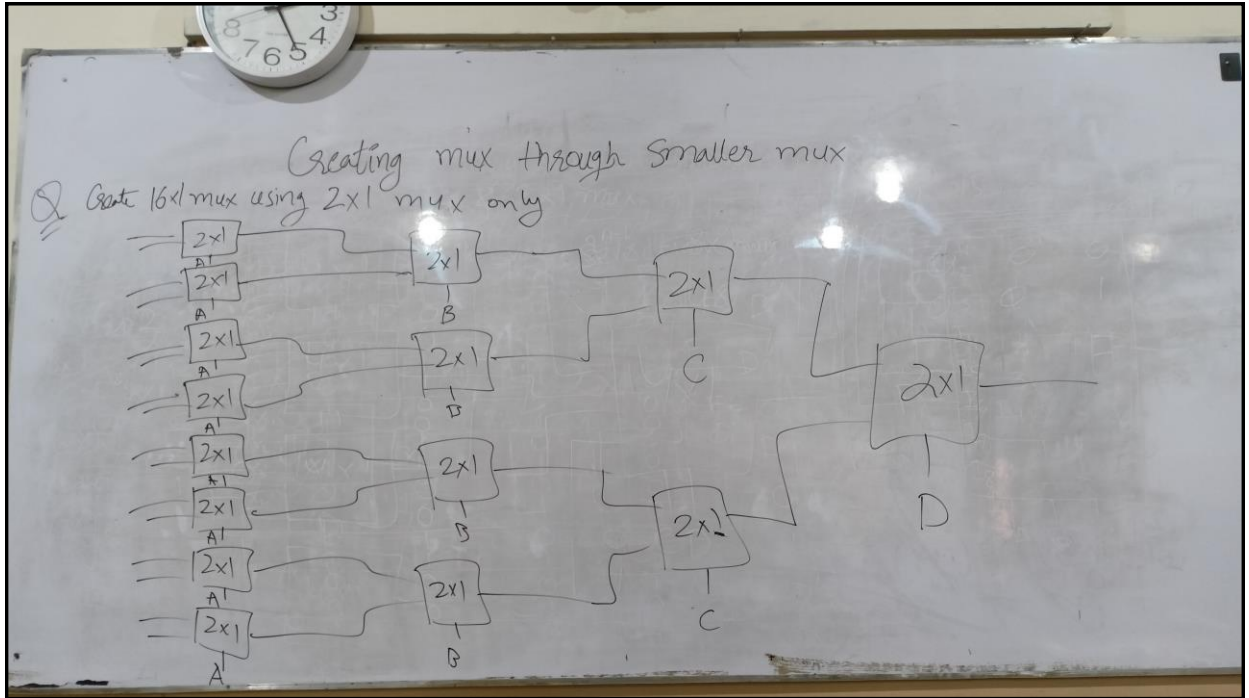


33

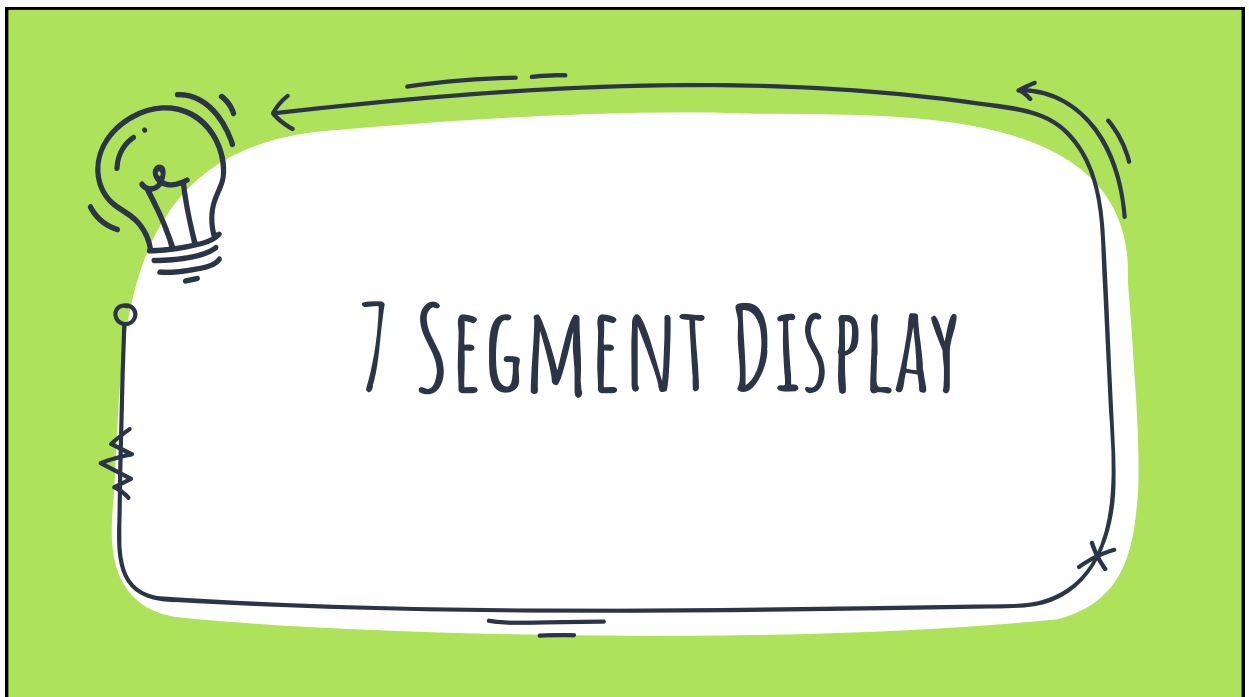

37

BCD TO 7 SEGMENT DISPLAY

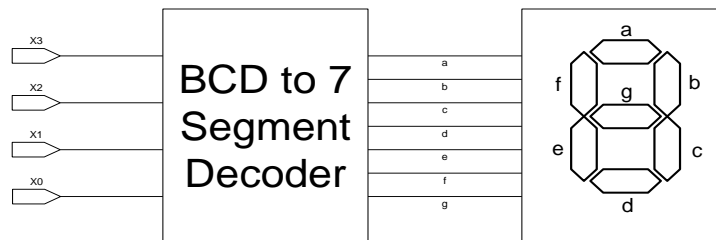


Design the logic circuitry that will drive a seven segment LED display and will be able to represent numbers from 0 to 9

38

38

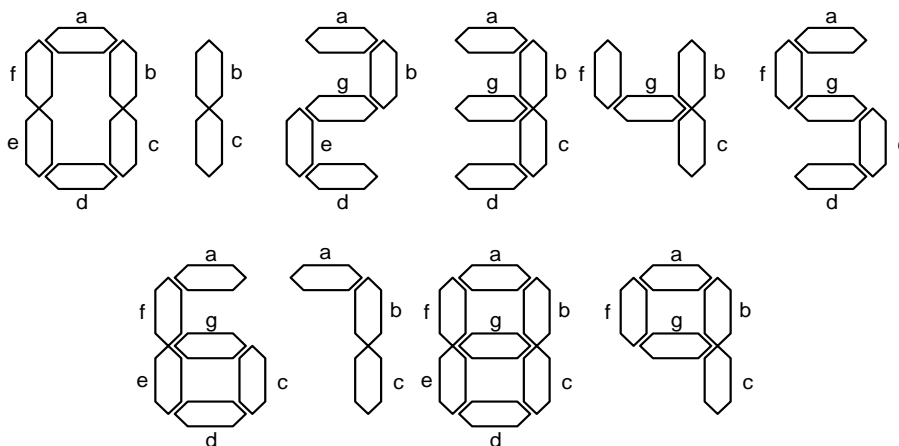POSSIBLE NUMBERS AND THEIR REPRESENTATION ON 7 SEGMENT DISPLAY



39

39

TRUTH TABLE

X3	X2	X1	X0	a	b	c	d	e	f	g
0	0	0	0	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1
0	0	1	1	1	1	1	1	0	0	1
0	1	0	0	0	1	1	0	0	1	1
0	1	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	1	1	1	1	1
0	1	1	1	1	1	1	0	0	0	0
1	0	0	0	1	1	1	1	1	1	1
1	0	0	1	1	1	1	0	0	1	1
1	0	1	0	x	x	x	x	x	x	x
1	0	1	1	x	x	x	x	x	x	x
1	1	0	0	x	x	x	x	x	x	x
1	1	0	1	x	x	x	x	x	x	x
1	1	1	0	x	x	x	x	x	x	x
1	1	1	1	x	x	x	x	x	x	x

40

40

REFERENCES

- X Chapter 4 – Digital Design Morris Mano
- X Logic and Computer Design Fundamentals, 4e, Power Point Slides, 2008 Pearson Education Inc.
- X Digital Design – Amirali Baniasad
- X Template is taken from slides carnival.

44